

---

# **C335**

## **Computer Structures**

### **ALU Design (II)**


Dr. Liqiang Zhang

Department of Computer and Information Sciences
 
# Review: A One Bit ALU


---

- ❑ This 1-bit ALU will perform AND, OR, and ADD



 
# Review: Logic Diagrams for CarryOut and Sum

❑  $\text{CarryOut} = B \cdot \text{CarryIn} + A \cdot \text{CarryIn} + A \cdot B$



 ❑  $\text{Sum} = A \text{ XOR } B \text{ XOR } \text{CarryIn}$




# Review: How About Subtraction?

❑ Keep in mind the followings:

- $(A - B)$  is the same as:  $A + (-B)$
- 2's Complement: Take the inverse of every bit and add 1



❑ Bit-wise inverse of B is  $B'$ :

 - $A + B' + 1 = A + (B' + 1) = A + (-B) = A - B$



 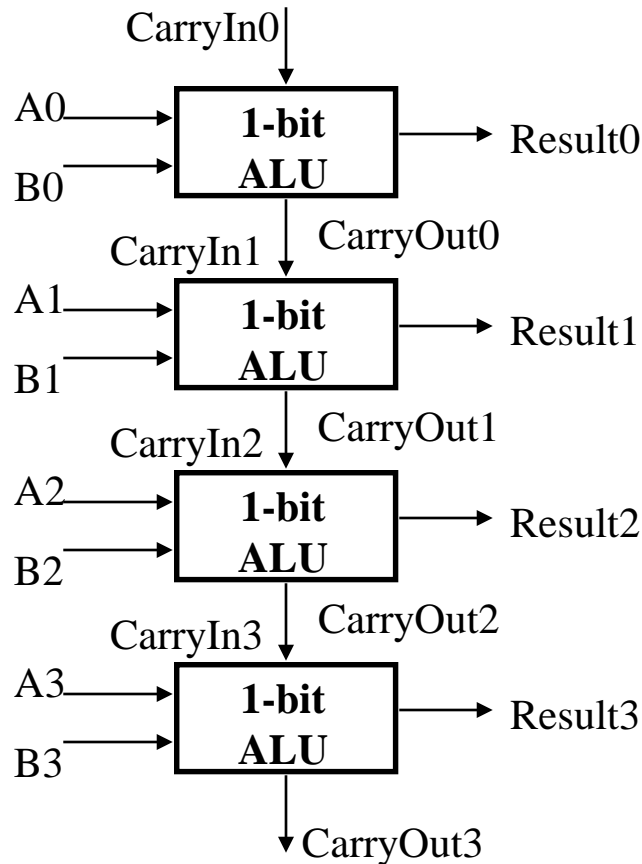
# Review: the Disadvantage of Ripple Carry

- ❑ The adder we just built is called a “Ripple Carry Adder”
  - The carry bit may have to propagate from LSB to MSB
  - Worst case delay for a N-bit adder:  $2N$ -gate delay



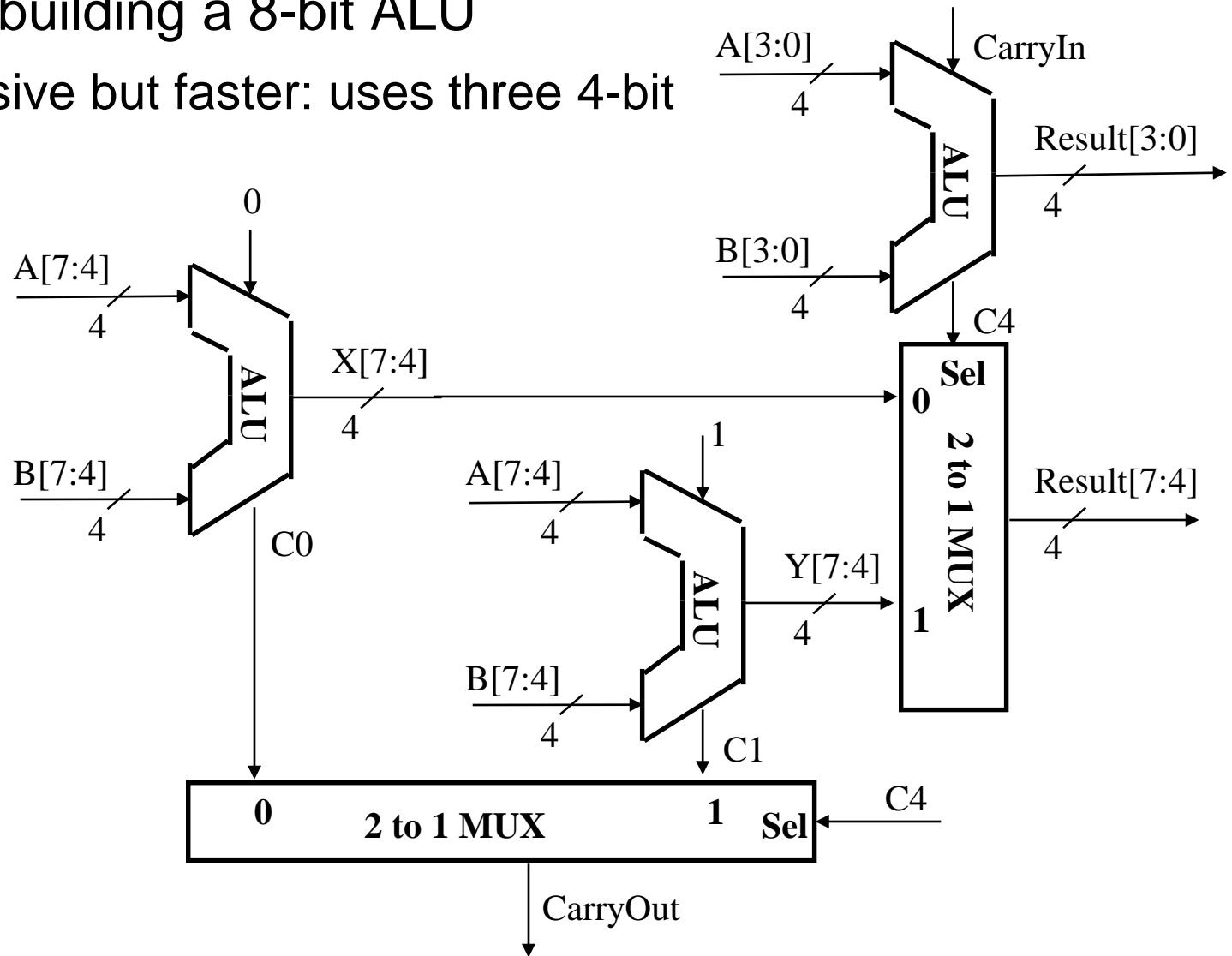
# Review: Carry Select Header

- ❑ Consider building a 8-bit ALU
  - Expensive but faster: uses three 4-bit ALUs


 
# Review: Functional Specification of the ALU



## □ ALU Control Lines (ALUOp)

## Function

● 000

And

● 001

Or

● 010

Add

● 110

Subtract

● 111

Set-on-less-than

# Deriving requirements of ALU

---

- ❑ Start with instruction set architecture: must be able to do all operations in ISA
- ❑ Tradeoffs of cost and speed based on the frequency of occurrence and hardware budget
- ❑ MIPS ISA



# MIPS ALU requirements

---



- ❑ Add, Sub, Addl  
=> 2's complement adder with overflow detection & inverter
- ❑ SLT, SLTI (set less than)  
=> 2's complement adder with inverter, check sign bit of result
- ❑ BEQ, BNE (branch on equal or not equal)  
=> 2's complement adder with inverter, check if result = 0
- ❑ And, Or, Andl, Orl  
=> Logical AND, logical OR
- ❑ ALU from last lecture supports these ops

# Additional MIPS ALU requirements

---

- ❑ Xor, Nor

=> Logical XOR, logical NOR or use 2 steps: (A OR B) XOR 1111....1111

- ❑ Sll, Srl, Sra


=> Need left shift, right shift, right shift arithmetic by 0 to 31 bits

- ❑ Mult, Div

=> Need 32-bit multiply and divide

# Add XOR to ALU


## Expand Multiplexer

 




Three different kinds:

 *logical*-- value shifted in is always "0"



 *arithmetic*-- on right shifts, sign extended



*rotating*-- shifted out bits are wrapped around (not in MIPS)



**Note: these are single bit shifts. A given instruction might request 0 to 31 bits to be shifted!**

# MIPS Multiply Instruction

- ❑ Multiply produces a 64-bit product

`mult $s0, $s1`      # `hi || lo = $s0 * $s1`

`multu $s0, $s1`      # `hi || lo = $s0 * $s1`

<code>op</code>	<code>rs</code>	<code>rt</code>	<code>rd</code>	<code>shamt</code>	<code>funct</code>
-----------------	-----------------	-----------------	-----------------	--------------------	--------------------

- Low-order word of the product is left in processor register `lo` and the high-order word is left in register `hi`
- Instructions `mfhi rd` and `mflo rd` are provided to move the product to (user accessible) registers in the register file

- ❑ Multiplies are done by fast, dedicated hardware and are much more complex (and slower) than adders

# MULTIPLY



## ❑ Paper and pencil example:

Multiplicand	1000
Multiplier	x 1001
	<hr/>
	1000
	0000
	0000
	1000
	<hr/>
Product	1001000

## ❑ $m$ bits $\times$ $n$ bits = $m+n$ bit product

## ❑ Binary makes it easy:


- 0  $\Rightarrow$  place 0 ( 0  $\times$  multiplicand)
- 1  $\Rightarrow$  place a copy of multiplicand ( 1  $\times$  multiplicand)

## ❑ 3 versions of multiply hardware & algorithm: successive refinement.

## ❑ Suppose, for now, multiply only positive numbers!


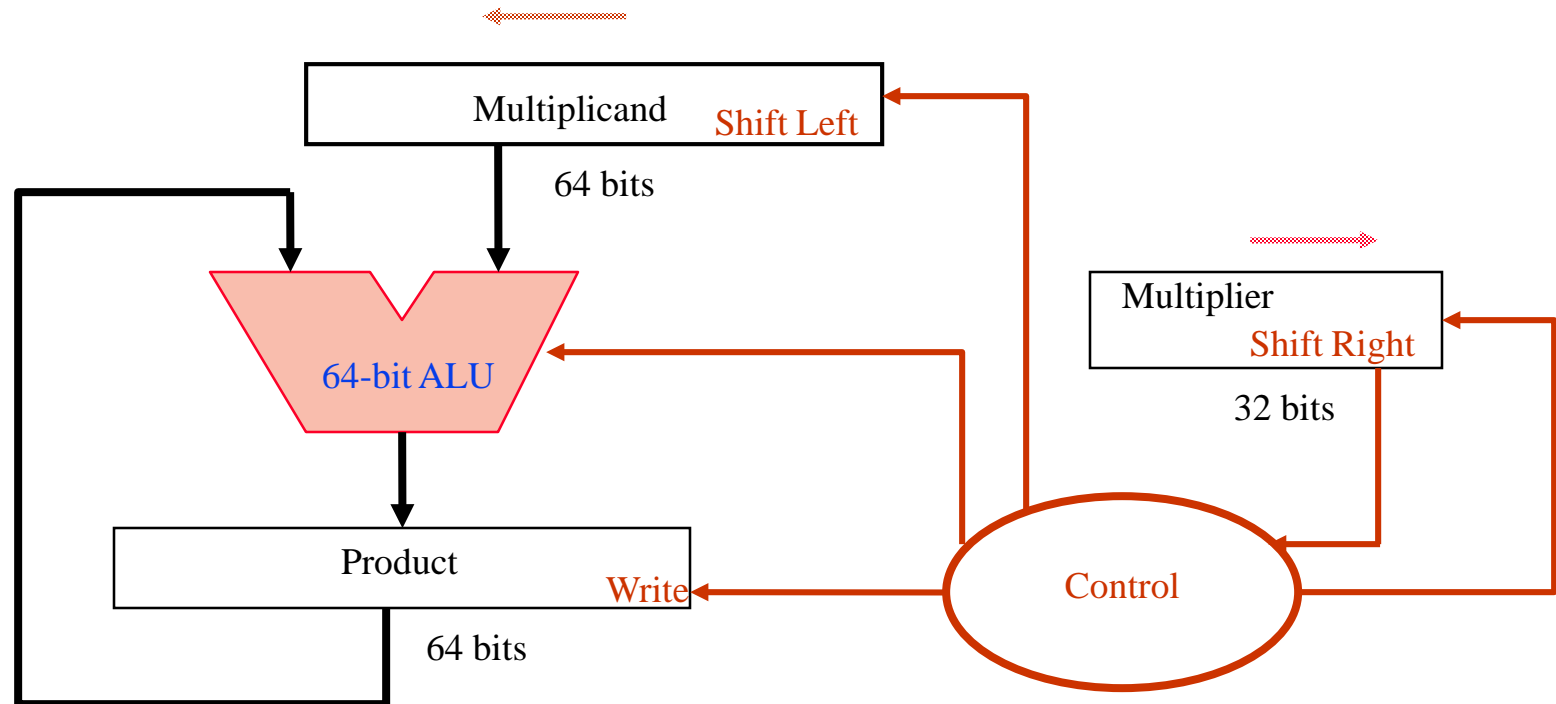
# MULTIPLY HARDWARE Version 1

- ❑ 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg




# Multiply Algorithm Version 1

Multiplier	Multiplicand	Product
0011	0000 0010	0000 0000

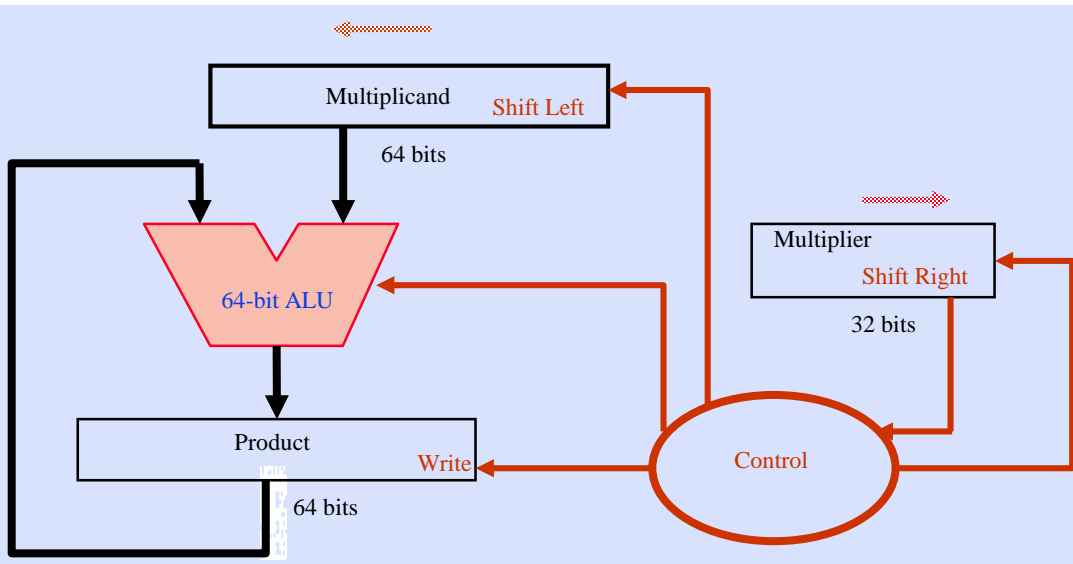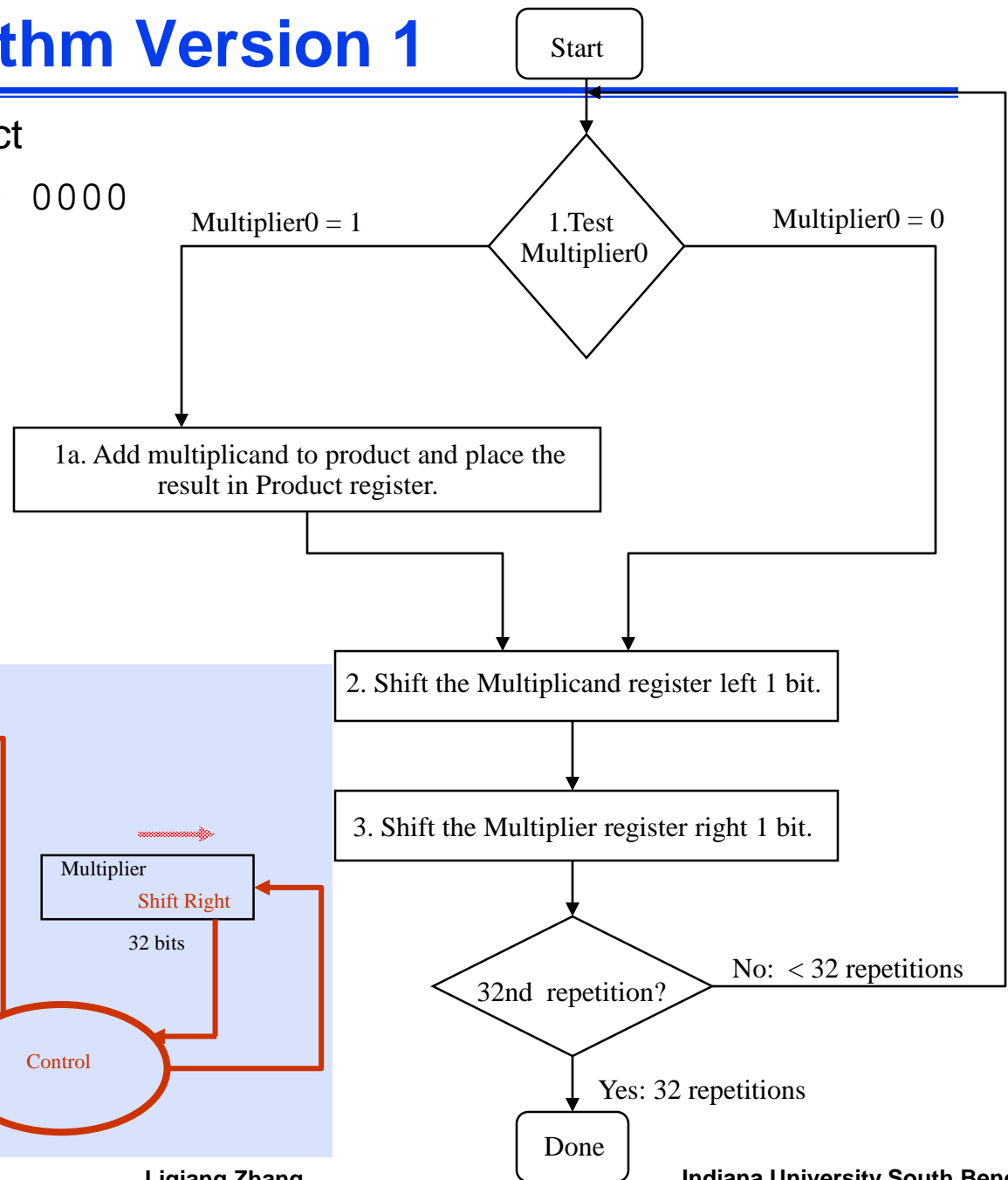




# Observations on Multiply Version 1

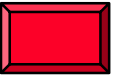

- ❑ 1 step per clock cycle  $\Rightarrow \approx 100$  clocks per multiply
  - Ratio of multiply to add/sub operations: 1:5 to 1:100
- ❑ 1/2 bits in multiplicand always 0  
 $\Rightarrow$  the full 64-bit adder is wasteful and slow, since half of the adder bits are adding 0 to the intermediate sum
- ❑ 0's inserted in right of multiplicand as shifted  
 $\Rightarrow$  least significant bits of product never changed once formed
- ❑ Instead of shifting multiplicand to left, shift product to right?
- ❑ 32-bit ALU and multiplicand

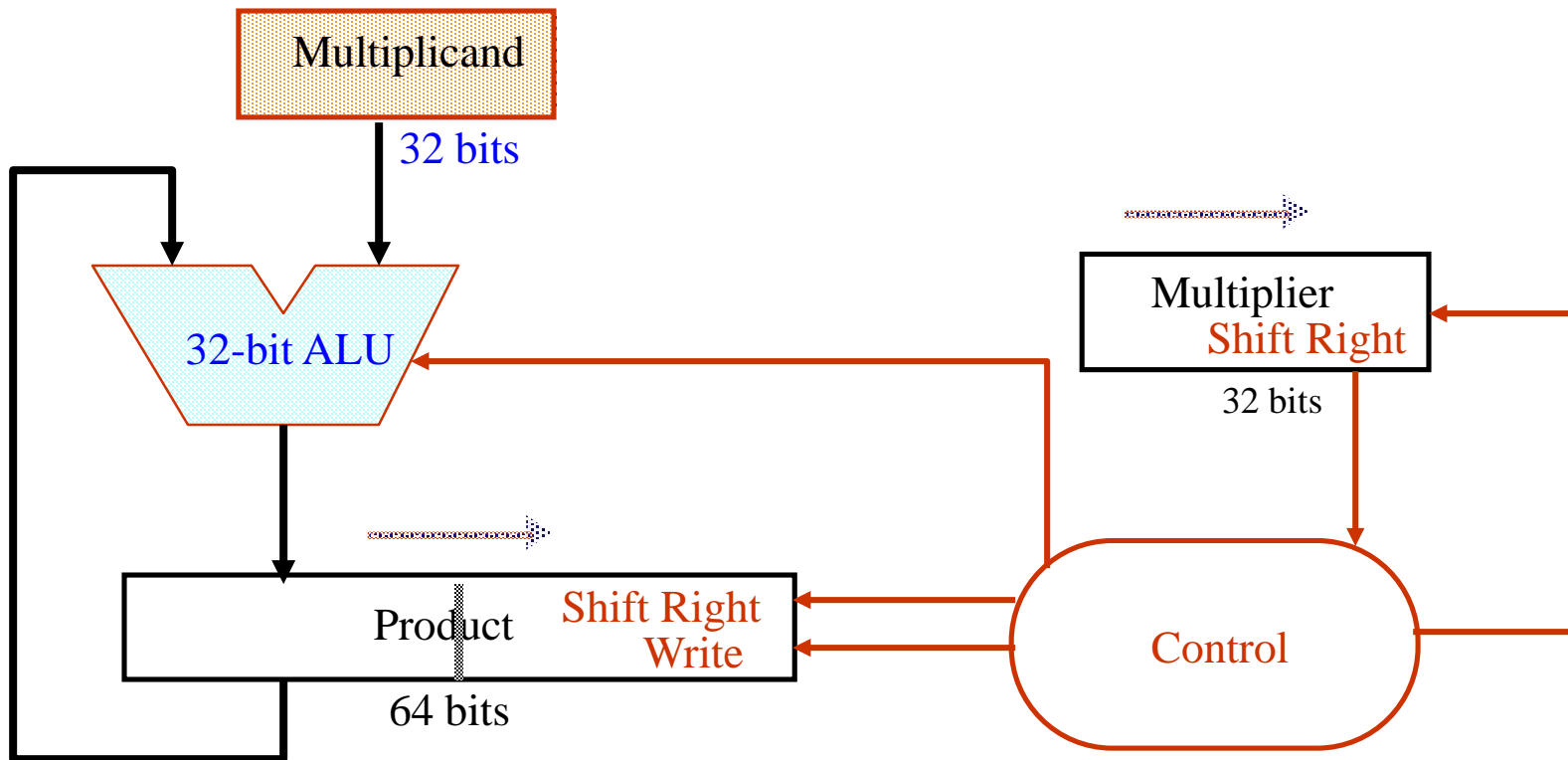
# MULTIPLY HARDWARE Version 2

- ❑ 32-bit Multiplicand reg, 32 -bit ALU, 64-bit Product reg, 32-bit Multiplier reg



# Multiply Algorithm Version 2

Multiplier	Multiplicand	Product
0011	0010	0000 0000

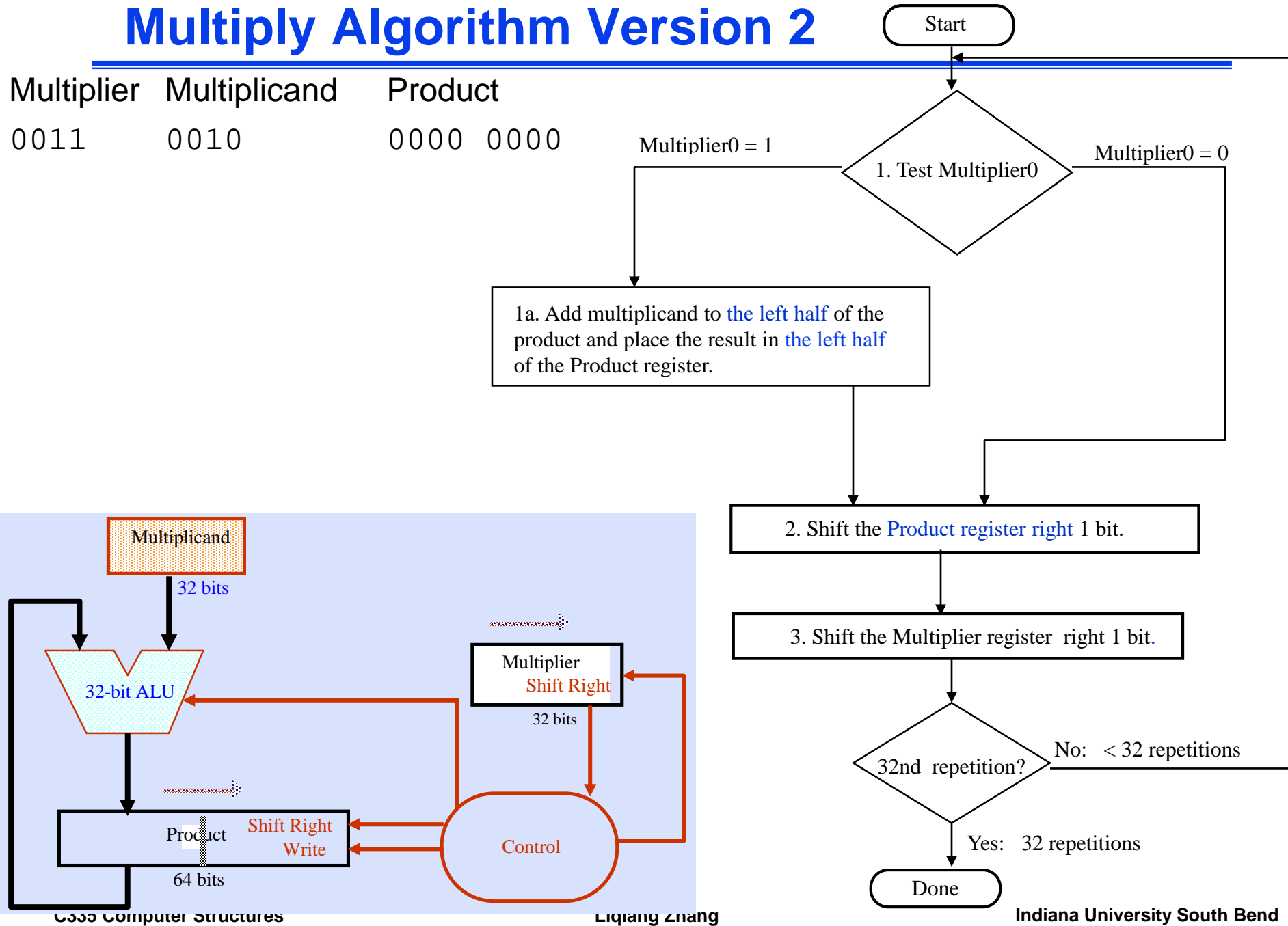

# Observations on Multiply Version 2


---



- ❑ Product register wastes space that exactly matches size of multiplier
- ❑ As the wasted space in product disappears, so do the bits of the multiplier.
- ❑ Thus, combine Multiplier register and Product register


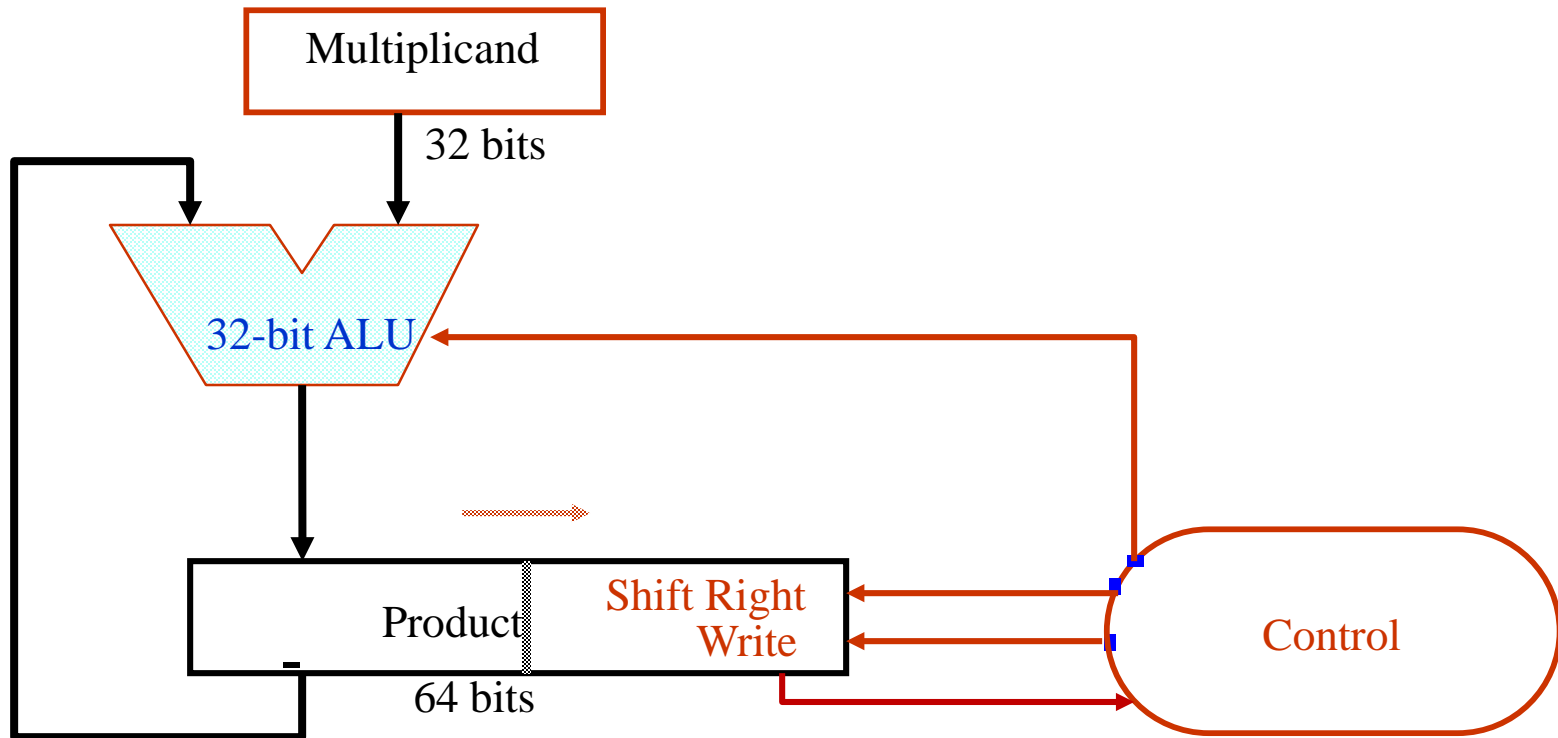
# MULTIPLY HARDWARE Version 3

- ❑ 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)


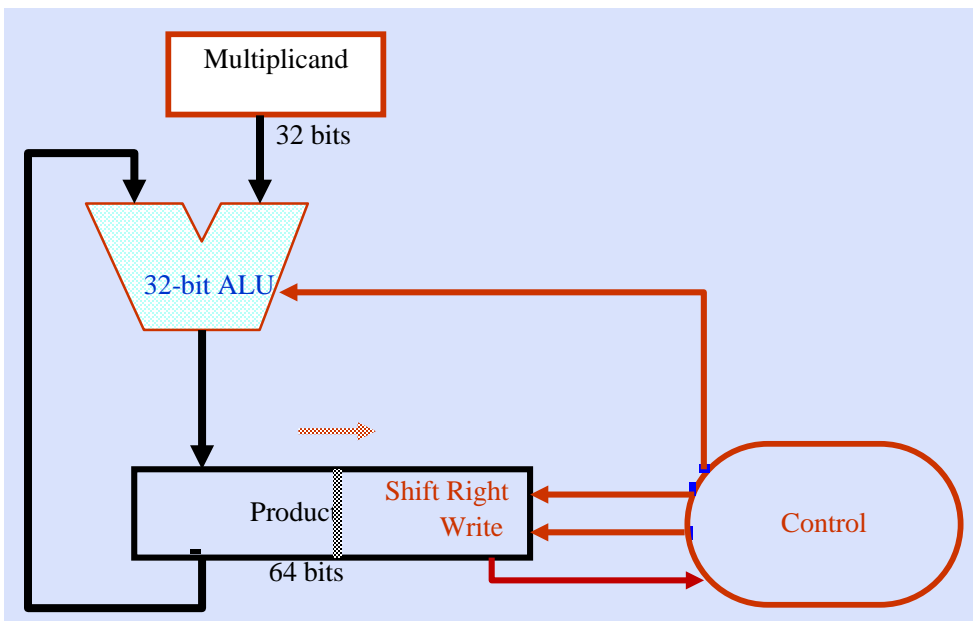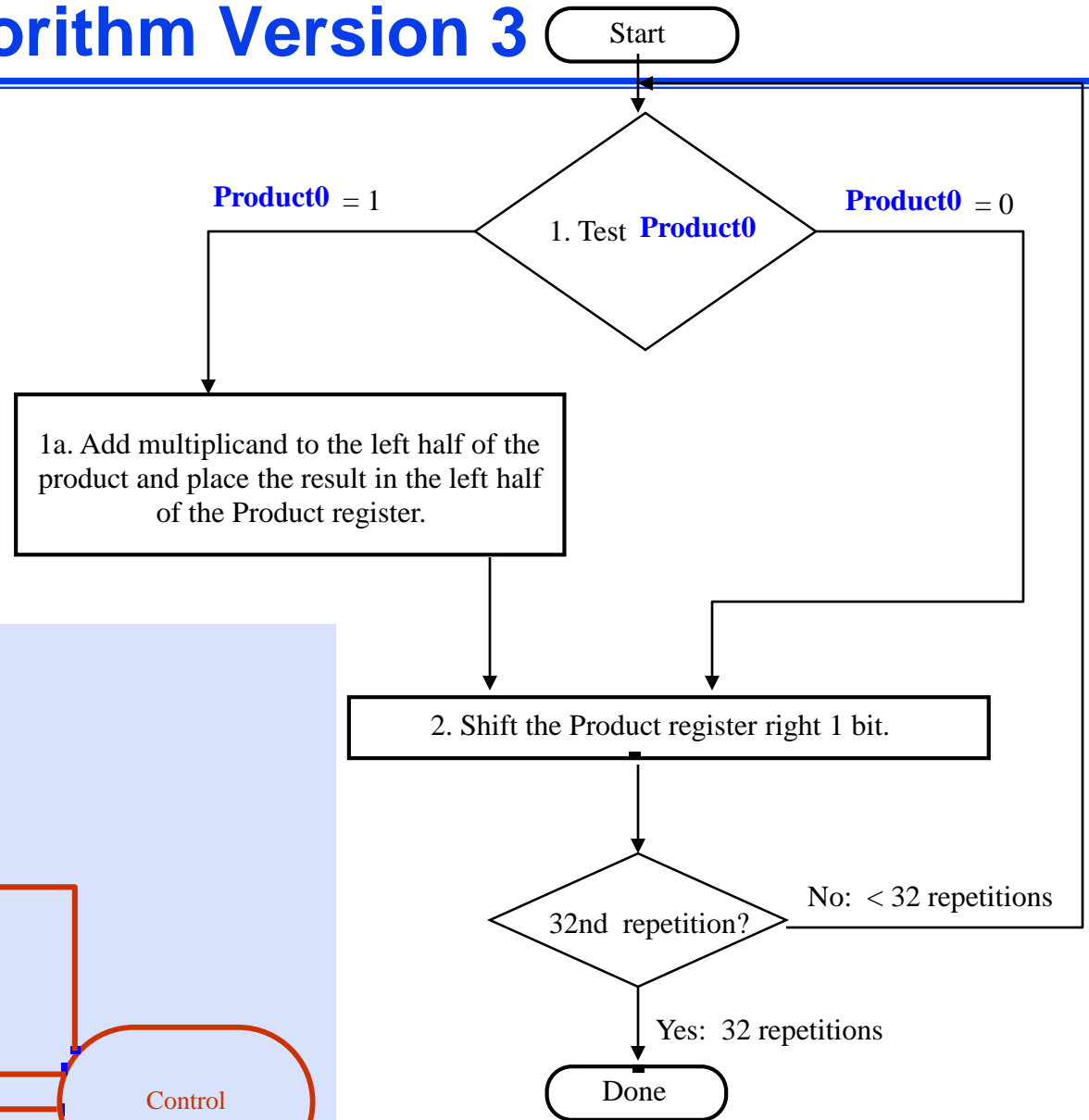
# Multiply Algorithm Version 3

Multiplicand    Product  
0010            0000 0011



# Observations on Multiply Version 3

---



- ❑ 2 steps per bit because Multiplier & Product combined, reducing instruction steps considerably!
- ❑ MIPS registers Hi and Lo are left and right half of Product
- ❑ Gives us MIPS instruction Multu
- ❑ What about signed multiplication?
  - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
  - Booth's Algorithm is more elegant way to multiply signed numbers using same hardware as before.

# Motivation for Booth's Algorithm



- Example  $2 \times 6 = 0010 \times 0110$ :

	0010	
x	0110	
<hr/>		
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
<hr/>		
	00001100	

- ALU with add or subtract can get the same result in more than one way:

$$6 = -2 + 8, \text{ or}$$
$$0110 = -0010 + 1000$$


- Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one. For example,

	0010	
x	0110	
<hr/>		
+	0000	shift (0 in multiplier)
-	0010	sub (first 1 in multiplier)
+	0000	shift (middle of string of 1s)
+	0010	add (prior step had last 1)
<hr/>		
	00001100	



# Booth's Algorithm Insight

---

 

Current Bit	Bit to the Right	Explanation	Example
1	0	Beginning of a run of 1s	000111 <u>1</u> 000
1	1	Middle of a run of 1s	00011 <u>1</u> 1000
0	1	End of a run of 1s	000 <u>1</u> 111000
0	0	Middle of a run of 0s	00 <u>0</u> 1111000

Originally for Speed since shift faster than add for this machine

For some bit patterns the algorithm is faster, it handles signed numbers too. In what case is Booth's algorithm not so desirable?

# Booth's Algorithm

1. Depending on the current bit and the bit to the right, which was the current bit in the previous step, do one of the following:
  - 00: a. Middle of a string of 0s, so no arithmetic operation.
  - 01: b. End of a string of 1s, so add the multiplicand to the left half of the product.
  - 10: c. Beginning of a string of 1s, so subtract the multiplicand from the left half of the product.
  - 11: d. Middle of a string of 1s, so no arithmetic operation.
2. As in the previous algorithm, shift the Product register right (arith.) 1 bit.

**Multiplicand      Product (2 x 3)**  
 0010            0000   0011   0

**Multiplicand**    **Product (2 x -3)**  
 0010            0000 1101 0

**Assume a rightmost bit of 0 to initialize the algorithm.**

# If you are Interested

---

❑ Using booth's algorithm to do the following calculations:

❑ Multiplicand	Multiplier
----------------	------------

❑ -2	3
------	---

❑ 2	-3
-----	----


❑ -2	-3
------	----

❑ 2	-8
-----	----


❑ -8	3
------	---

❑ Does it work well for all these cases?

# Faster Multiplier

 


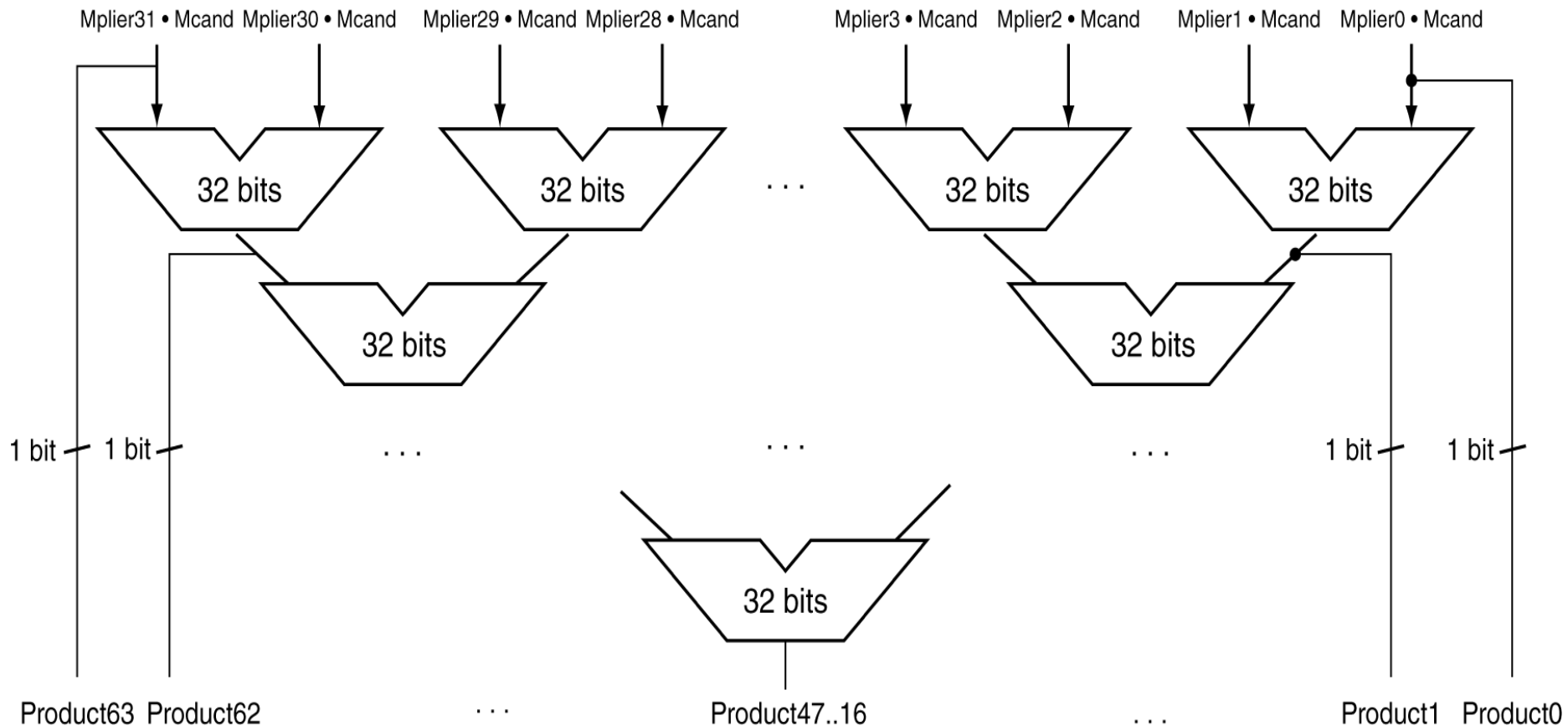- ❑ Uses multiple adders
- Cost/performance tradeoff


 
# Division

- Division is just a *bunch* of quotient digit guesses and left shifts and subtracts



# MIPS Divide Instruction



- Divide generates the remainder in `hi` and the quotient in `lo`

```
div    $s0, $s1          # lo = $s0 / $s1
                        # hi = $s0 mod $s1
```

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------

- Instructions `mflo rd` and `mfhi rd` are provided to move the quotient and remainder to (user accessible) registers in the register file

# Divide: Paper & Pencil

---

Divisor 1000	$\overline{)1001010}$	Quotient
		Dividend

# Divide: Paper & Pencil

---


	1001	Quotient
Divisor 1000	<div>1001010</div>	Dividend
	<div>-1000</div>	
	10	
	101	
	1010	
	<div>-1000</div>	
	10	Remainder

- ❑ See how big a number can be subtracted, creating quotient bit on each step
  - Binary  $\Rightarrow$   $1 * \text{divisor}$  or  $0 * \text{divisor}$
- ❑ Dividend = Quotient x Divisor + Remainder
- ❑ 3 versions of divide, successive refinement


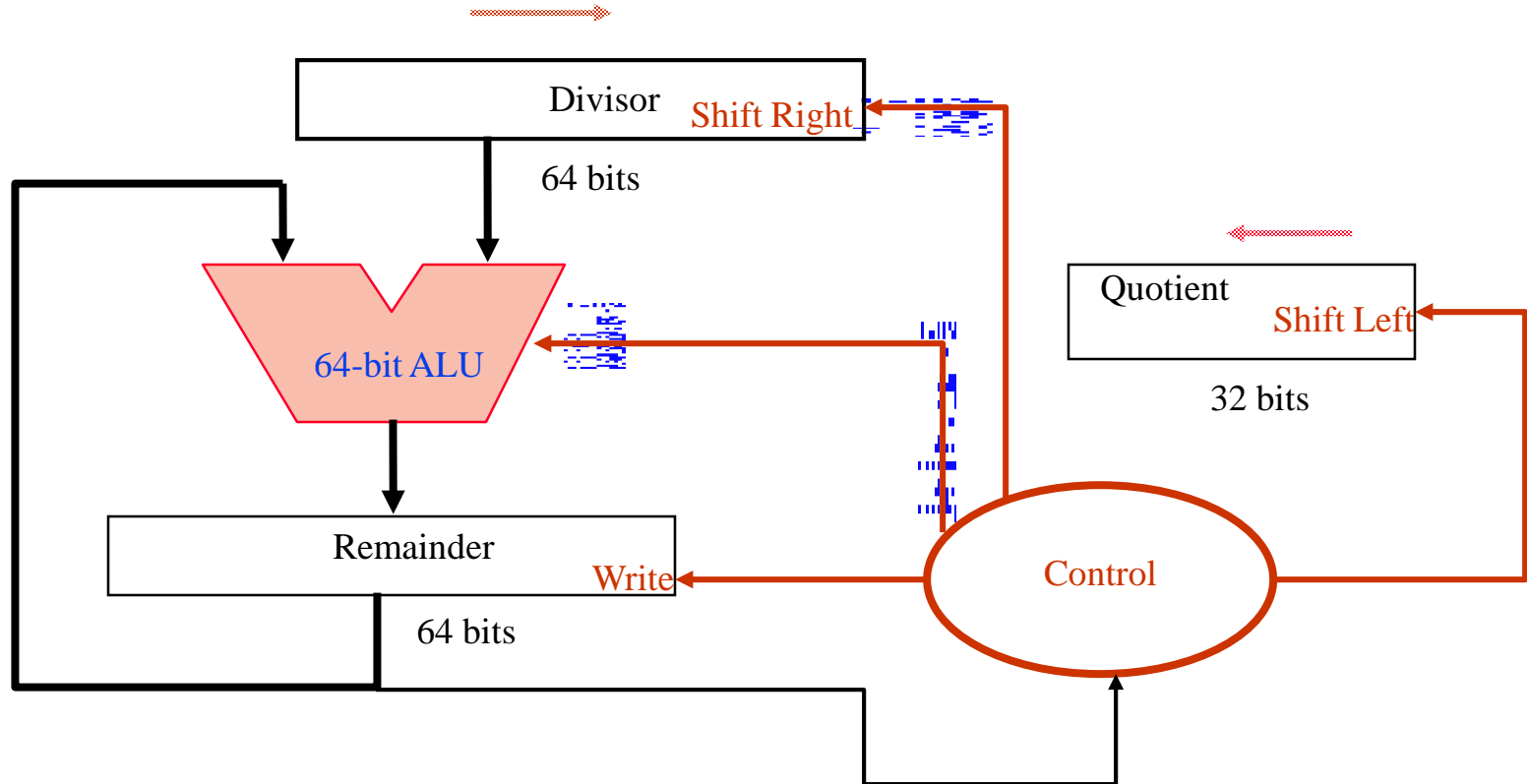
# DIVIDE HARDWARE Version 1


- ❑ 64-bit Divisor reg, 64-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg



# Divide Algorithm Version 1

❑ Takes  $n+1$  steps for  $n$ -bit Quotient & Rem.

Quotient	Divisor	Remainder
0000	0010	0000 0111

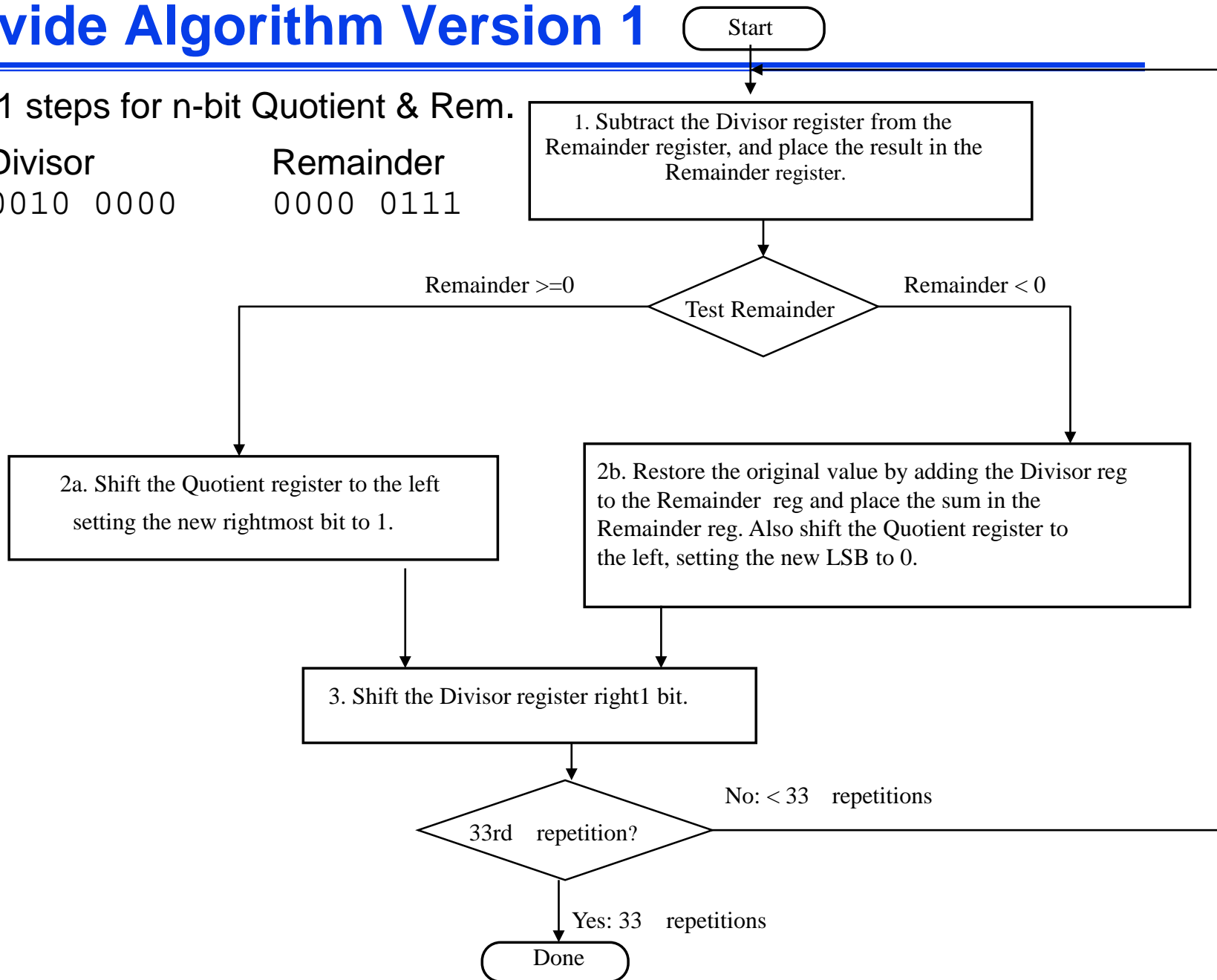

# Observations on Divide Version 1


---



- ❑ 1/2 bits in divisor always 0
  - => 1/2 of 64-bit adder is wasted
  - => 1/2 of divisor is wasted
- ❑ Instead of shifting divisor to right, shift remainder to left?
- ❑ 1st step cannot produce a 1 in quotient bit (otherwise too big)
  - => switch order to shift first and then subtract, can save 1 iteration

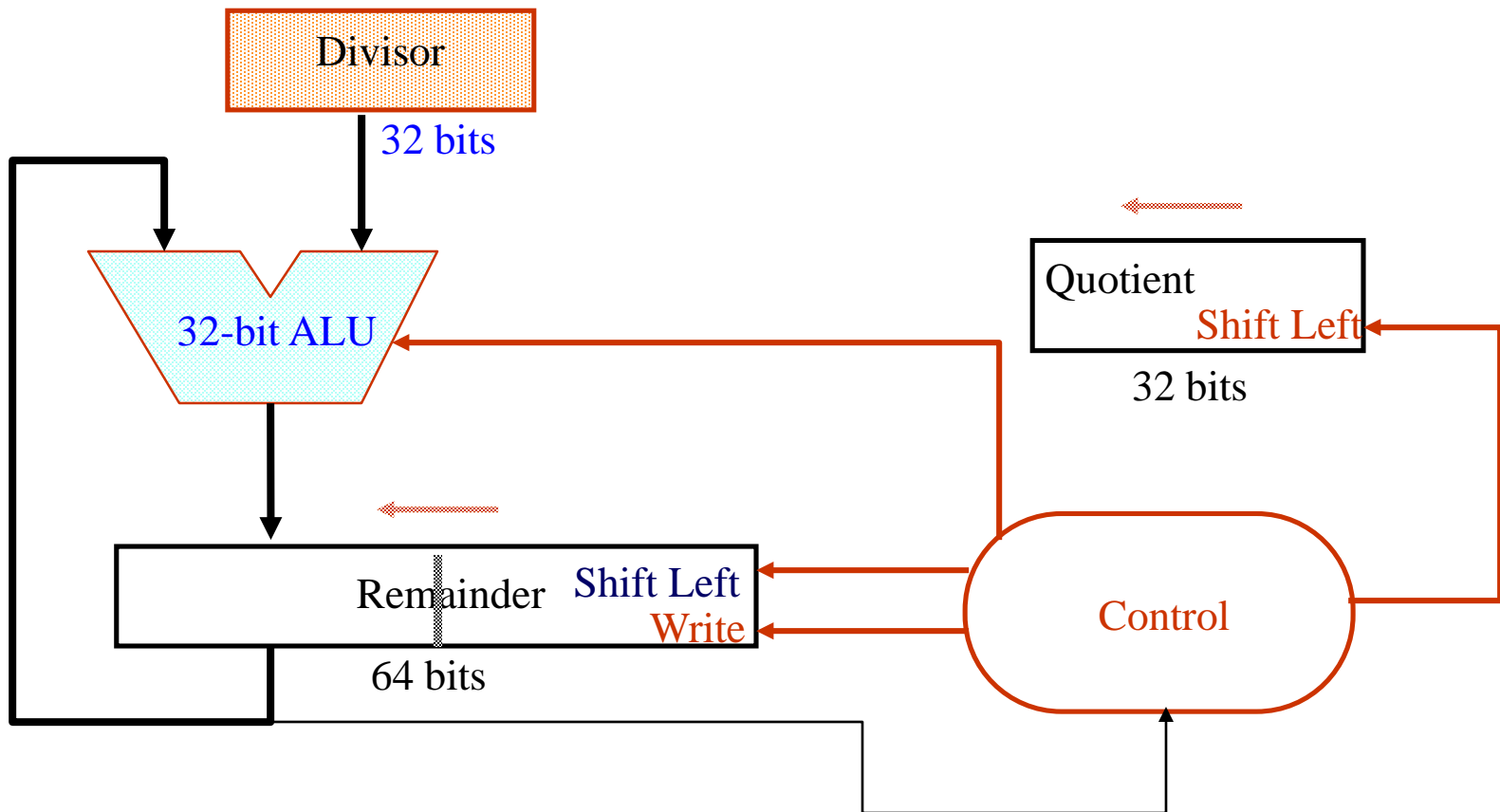
# DIVIDE HARDWARE Version 2

- ❑ 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg



# Divide Algorithm Version 2

Quotient	Divisor	Remainder
0000	0010	0000 0111

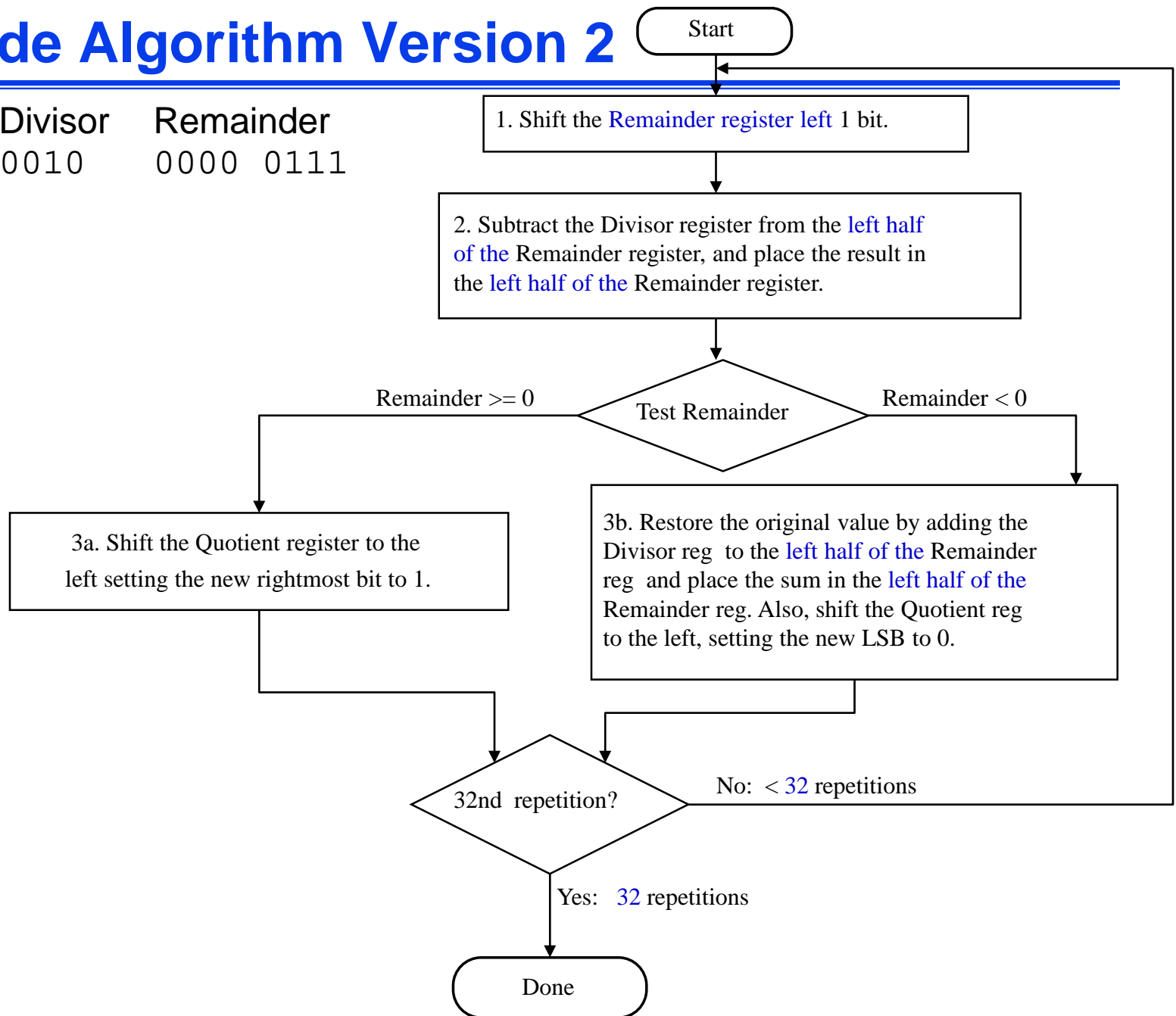




- ❑ Eliminate Quotient register by combining with Remainder as shifted left.
  - Start by shifting the Remainder left as before.
  - Thereafter loop contains only two steps because the shifting of the Remainder register shifts both the remainder in the left half and the quotient in the right half.
  - The consequence of combining the two registers together and the new order of the operations in the loop is that the remainder will be shifted left one time too many.
  - Thus the final correction step must shift back only the remainder in the left half of the register.

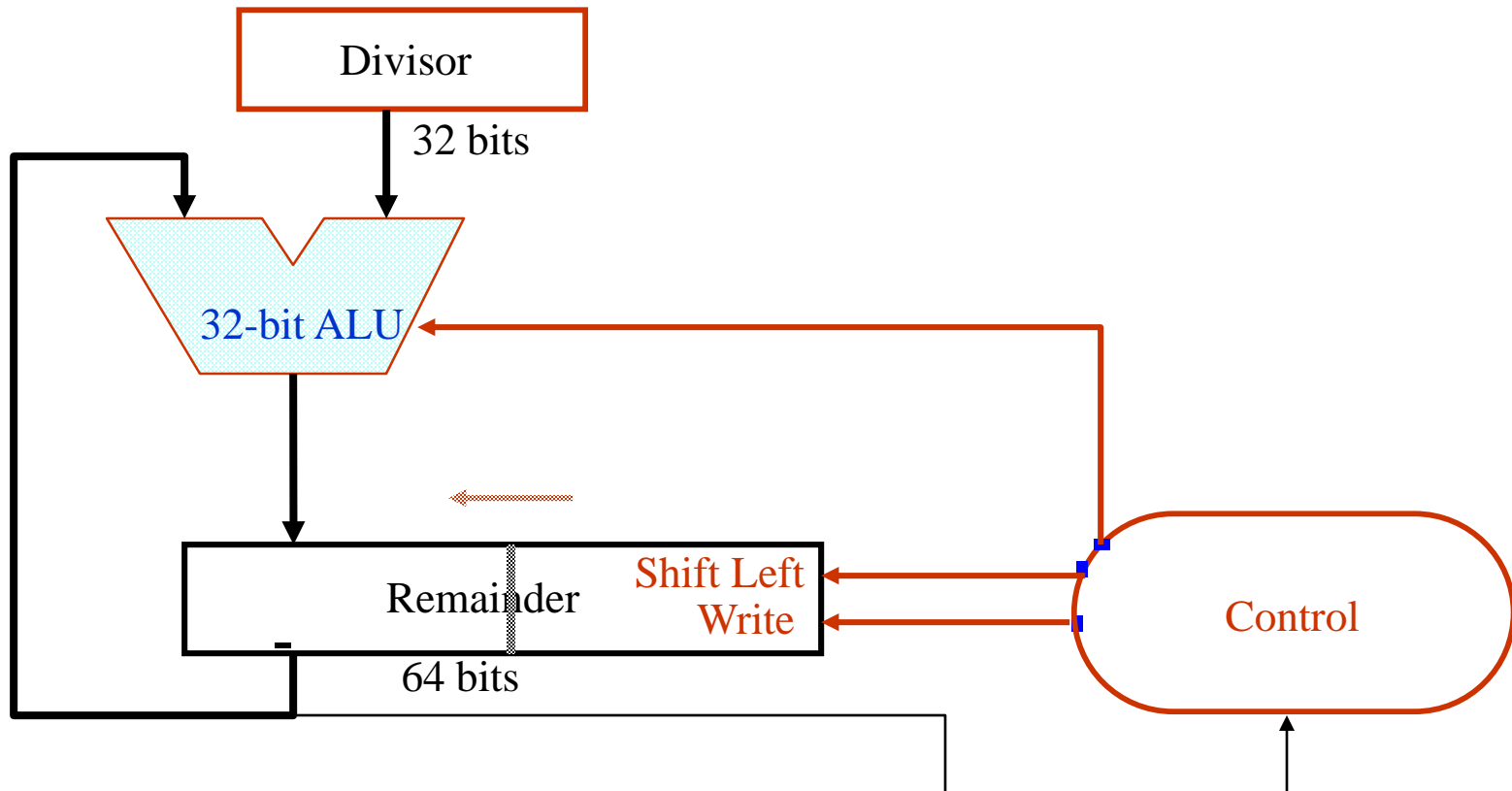
# DIVIDE HARDWARE Version 3

- ❑ 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, (0-bit Quotient reg)


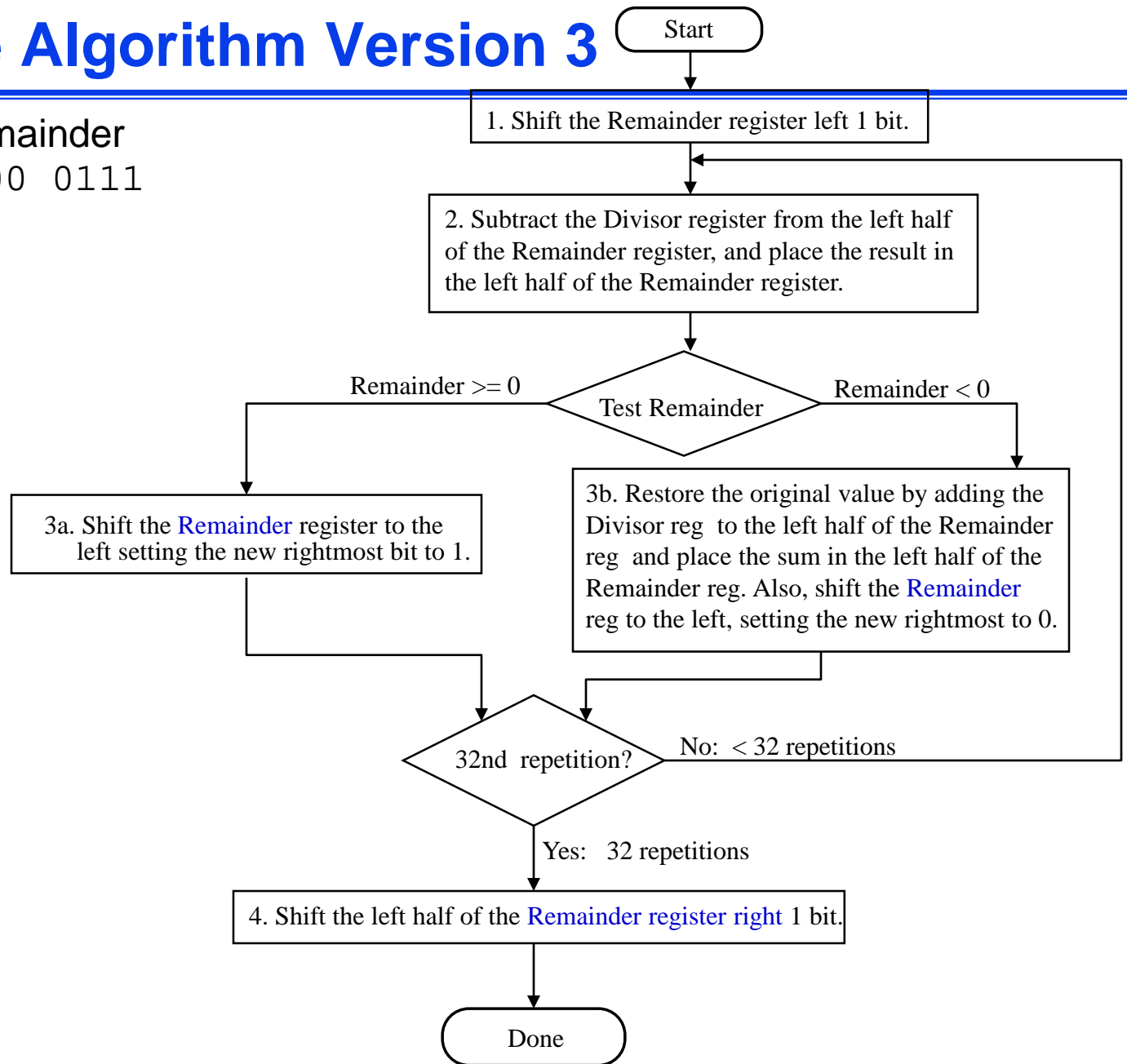
# Divide Algorithm Version 3

Divisor      Remainder  
0010      0000 0111





# Observations on Divide Version 3

---



- ❑ Same Hardware as Multiply: just need ALU to add or subtract, and 64-bit register to shift left or shift right
- ❑ Hi and Lo registers in MIPS combine to act as 64-bit register for multiply and divide
- ❑ Signed Divides: Simplest is to remember signs, make positive, and complement quotient and remainder if necessary

# Summary

---

- ❑ Instruction Set drives the ALU design
- ❑ Multiply: successive refinement to see final design
  - 32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register
  - Booth's algorithm to handle signed multiplies
- ❑ There are algorithms that calculate many bits of multiply per cycle
- ❑ Divide can use same hardware as multiply: Hi & Lo registers in MIPS.