
C335

Computer Structures

Mid Term Exam #2 Review

Dr. Liqiang Zhang

Department of Computer and Information Sciences

Introduction to Logic Design

- ❑ Boolean Algebra, Switching Algebra
- ❑ Gates, logic equations, truth table
- ❑ Properties of Boolean Algebra
 - Axioms, single-variable, two & three variable
 - De Morgan's theorem (**memorize**)
- ❑ Induction proof
- ❑ Canonical forms: Minterm and Maxterm
- ❑ The triangle relationship of ...
- ❑ Design of half adder, full adder
- ❑ Multiplexor, decoder

ALU Design

- ❑ One-bit ALU → 4-bit ALU
- ❑ Subtraction? Overflow? Zero detection?
- ❑ Ripple Carry adder
 - Disadvantages?
 - Enhancement?
 - Carry Select Header
 - Carry Lookahead
- ❑ Multiply
 - Three versions
 - Booth's algorithm
- ❑ Divide (basic idea?)
 - Three versions

CPU Design

- ❑ Strategy: break up into stages
 - How many? Do what in each?
 - CPU clocking
- ❑ Single-cycle datapath CPU design
 - Introduction of sequential logic
 - Latch and flip-flop
 - Other examples of state elements: register, register file, memory
 - Our implementation
 - Edge-triggered methodology
 - Typical execution
 - Stage-by-stage, instruction-by-instruction
 - Multiplexor insertion
 - timing

CPU Design

- ❑ Single-cycle datapath CPU design
 - Control unit design
 - Two level design
 - ALU control – how to?
 - Main control – how to?
 - Disadvantages of single-cycle design?
- ❑ Multi-cycle datapath CPU design