
C335

Computer Structures

ALU Design (I)

Dr. Liqiang Zhang

Department of Computer and Information Sciences

The Design is to Represent

(1) Functional Specification

Inputs: 2 x 16 bit operands- A, B; 1 bit carry input- Cin, 3 bit mode/function.


Outputs: 1 x 16 bit result- S; 1 bit carry output- Co.

Operations: SLT, ADD (A plus B plus Cin), SUB (A minus B minus Cin), AND, XOR, OR, COMPARE (equality)

Performance: left unspecified for now!

(2) Block Diagram


Understand the data and control flows

 


Review: Two's Complement Arithmetic

Decimal	Binary	Decimal	2's Complement
0	0000	0	0000
1	0001	-1	1111
2	0010	<u>-2</u>	<u>1110</u>
3	0011	-3	1101
4	0100	-4	1100
5	0101	<u>-5</u>	<u>1011</u>
6	0110	<u>-6</u>	<u>1010</u>
7	0111	-7	1001
		-8	1000


□ Examples: $7 - 6 = 7 + (-6) = 1$

 

$3 - 5 = 3 + (-5) = -2$

 

Block Diagram of the ALU

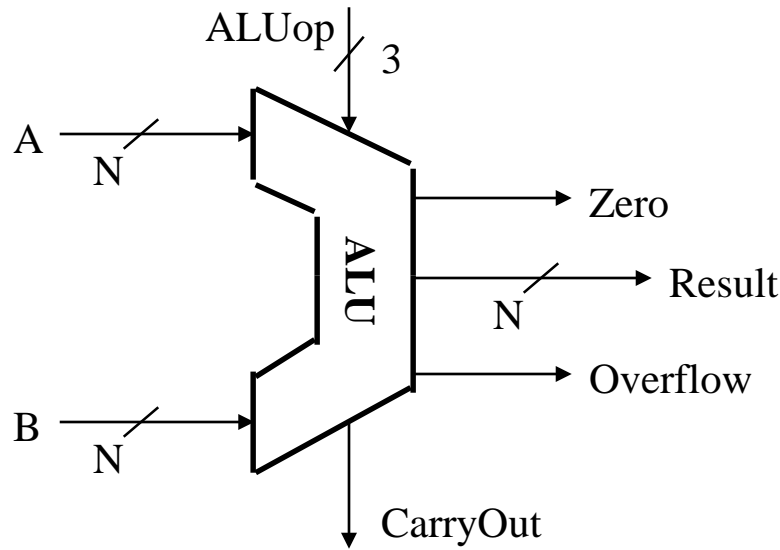

❑ ALU Control Lines (ALUOp)

• 000

• 001

• 010

• 110

• 111

Function

And

Or


Add

Subtract

Set-on-less-than


4 Hardware Building Blocks

- AND gate ($c = a \cdot b$)

 


a	b	$c = a \cdot b$
0	0	0
1	0	0
0	1	0
1	1	1

- OR gate ($c = a + b$)

 


a	b	$c = a + b$
0	0	0
1	0	1
0	1	1
1	1	1

- Inverter ($c = a'$)

 

a	$c = a'$
0	1
1	0

 
- Multiplexer
if $d=0$, $c=a$;
otherwise $c=b$



d	c
0	a
1	b


A One Bit ALU

 - ❑ This 1-bit ALU will perform AND, OR, and ADD



Review: A One-bit Full Adder

 
- ❑ **1 bit full adder:** a switching circuit which add together two binary digits (bits), and a third bit called a *CarryIn* bit which may have come from a previous full adder.




Inputs			Outputs		Comments
A	B	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00$
0	0	1	0	1	$0 + 0 + 1 = 01$
0	1	0	0	1	$0 + 1 + 0 = 01$
0	1	1	1	0	$0 + 1 + 1 = 10$
1	0	0	0	1	$1 + 0 + 0 = 01$
1	0	1	1	0	$1 + 0 + 1 = 10$
1	1	0	1	0	$1 + 1 + 0 = 10$
1	1	1	1	1	$1 + 1 + 1 = 11$

Review: A One-bit Full Adder

 
- $\text{Sum} = A \oplus B \oplus \text{CarryIn}$
- $\text{CarryOut} = B \cdot \text{CarryIn} + A \cdot \text{CarryIn} + A \cdot B$




A 4-bit ALU

 


1-bit ALU

 

4-bit ALU

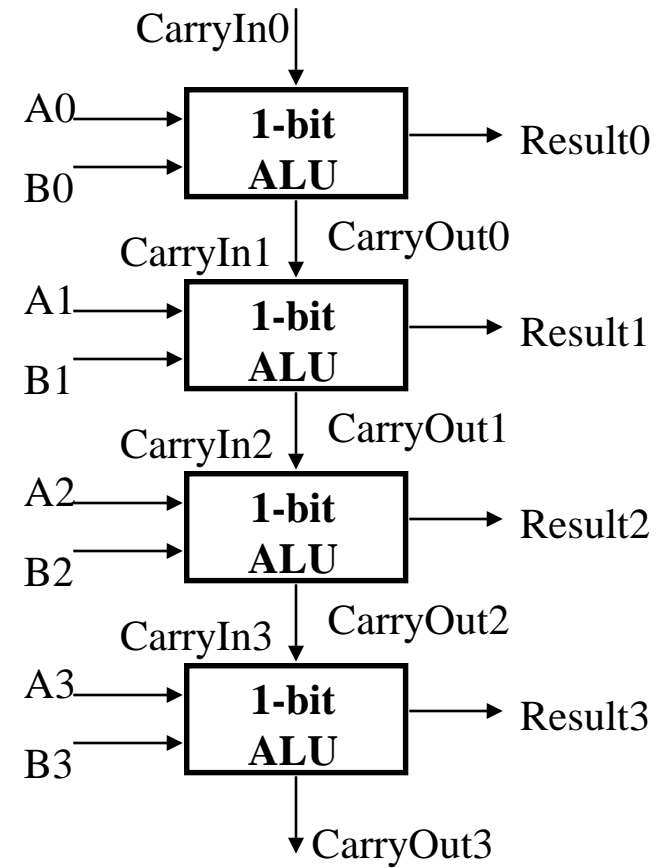

How About Subtraction?

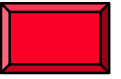


❑ Keep in mind the followings:

- (A - B) is the that as: $A + (-B)$
- 2's Complement: Take the inverse of every bit and add 1

❑ Bit-wise inverse of B is B':

 - $A + B' + 1 = A + (B' + 1) = A + (-B) = A - B$







Overflow


Decimal	Binary	Decimal	2's Complement
0	0000	0	0000
1	0001	-1	1111
2	0010	-2	1110
3	0011	-3	1101
4	0100	-4	1100
5	0101	-5	1011
6	0110	-6	1010
7	0111	-7	1001
		-8	1000

❑ Examples: $7 + 3 = 10$ but ...



$-4 - 5 = -9$ but ...

  

Overflow Detection

 

- ❑ Overflow: the result is too large (or too small) to represent properly
 - Example: $-8 \leq 4\text{-bit binary number} \leq 7$
- ❑ Can overflow happen when adding operands with different signs?
- ❑ Overflow occurs when adding:
 - 2 positive numbers and the sum is negative
 - 2 negative numbers and the sum is positive
- ❑ Exercise: Prove you can detect overflow by:
 - Carry into MSB \neq Carry out of MSB

  


Overflow Detection Logic




❑ Carry into MSB \neq Carry out of MSB

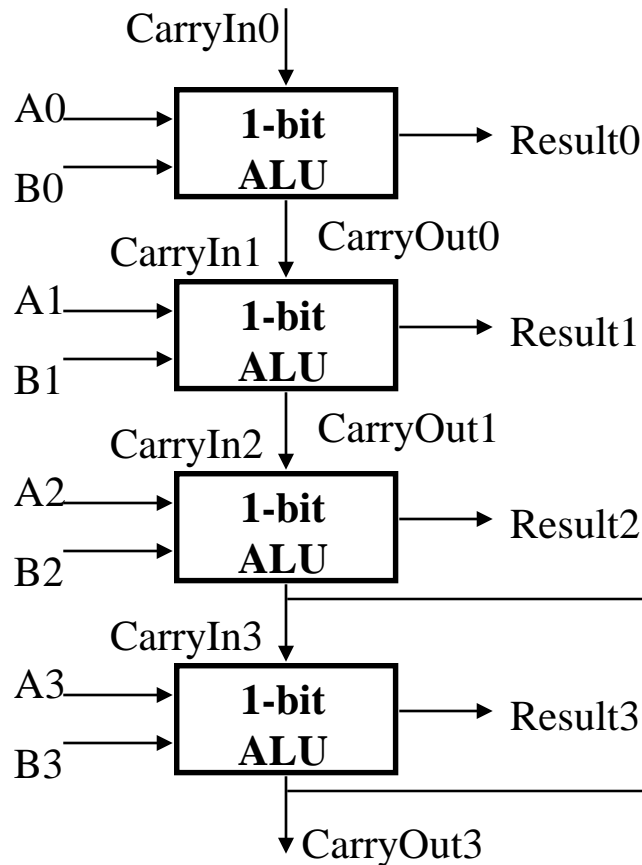
- For a N-bit ALU: $\text{Overflow} = \text{CarryIn}[N - 1] \text{ XOR } \text{CarryOut}[N - 1]$




X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

 

Zero Detection Logic


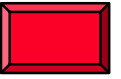


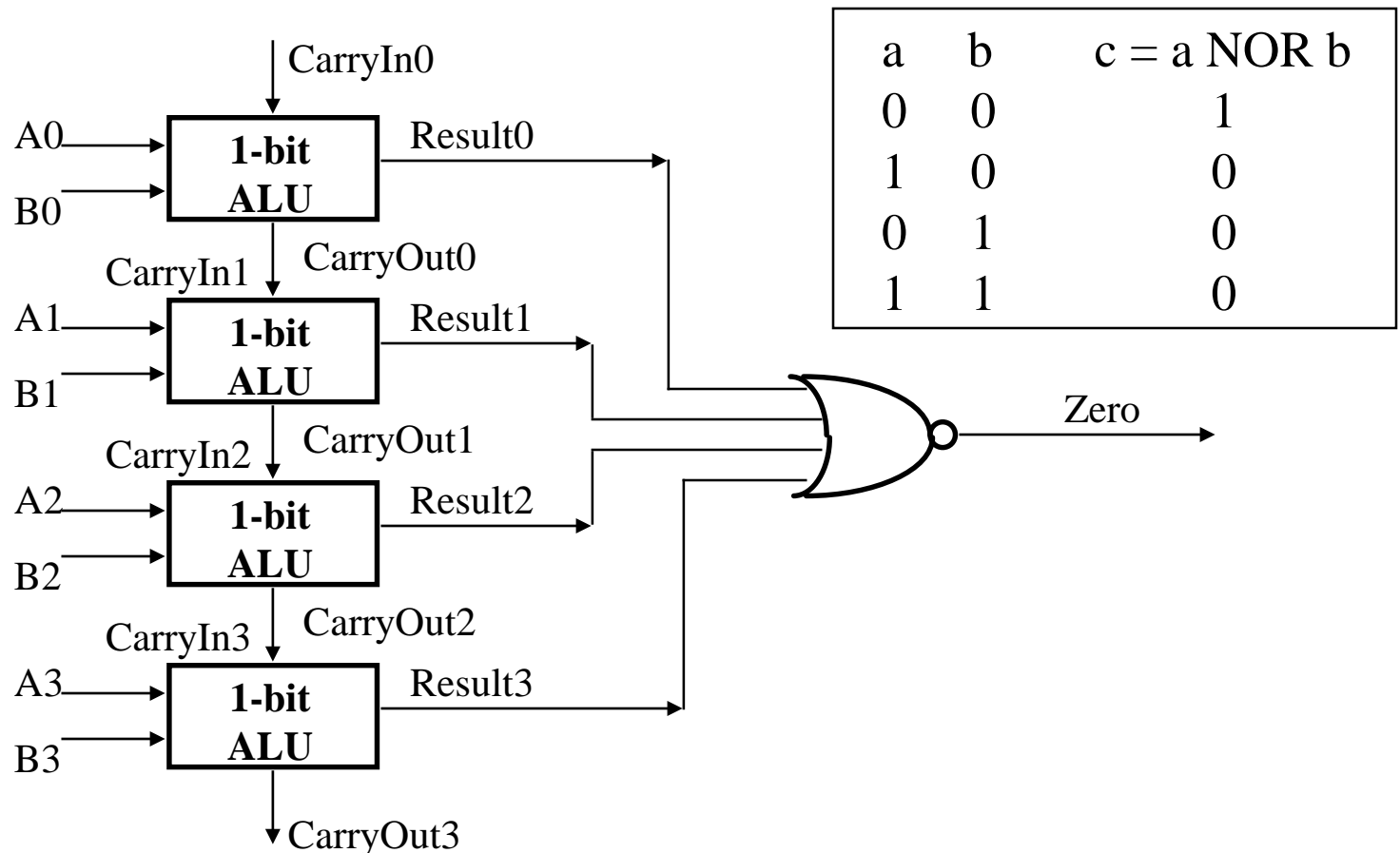- ❑ $A = B$ is the same as $A - B = 0$
- ❑ Zero Detection Logic is just a one BIG NOR gate
 - Any non-zero input to the NOR gate will cause its output to be zero




The Disadvantage of Ripple Carry

 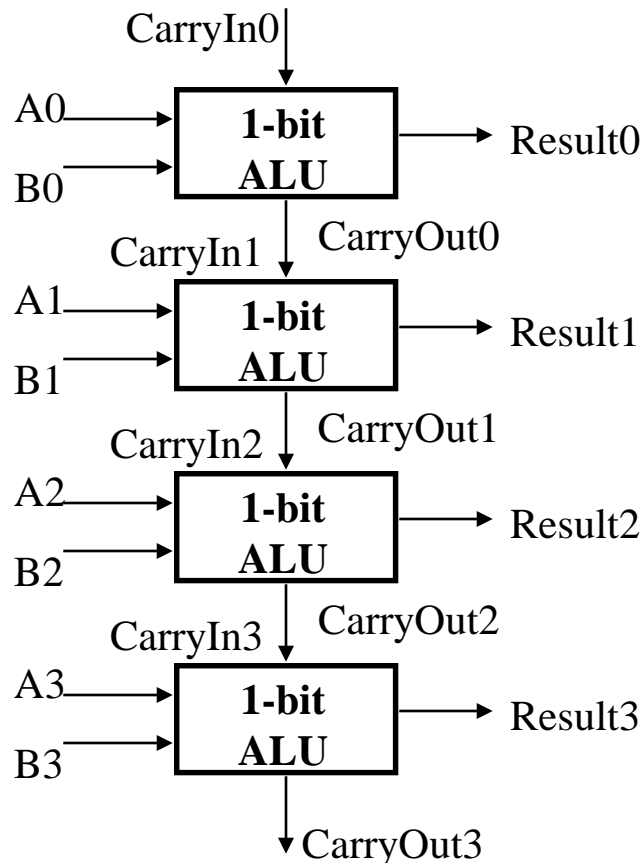- ❑ The adder we just built is called a “Ripple Carry Adder”
 - The carry bit may have to propagate from LSB to MSB
 - Worst case delay for a N-bit adder: $2N$ -gate delay




Carry Select Header

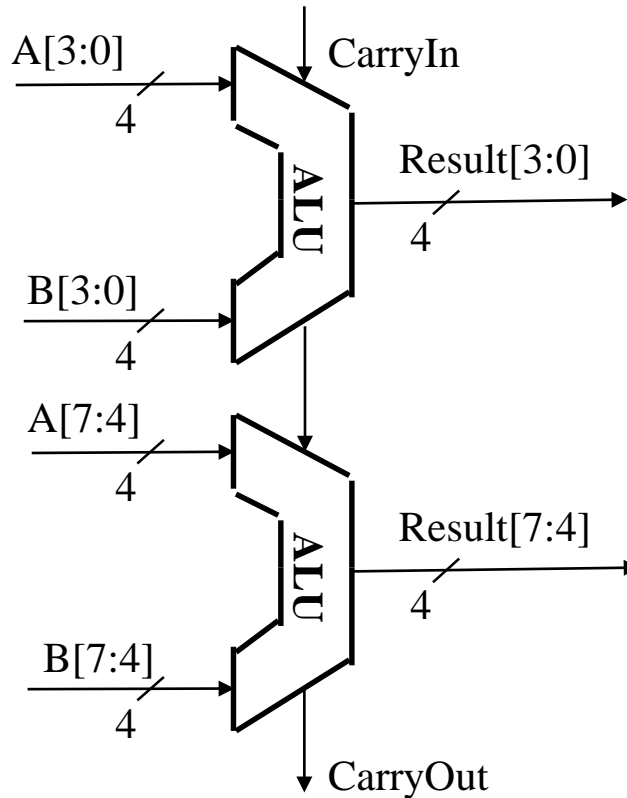- ❑ Consider building a 8-bit ALU
 - Simple: connects two 4-bit ALUs in series




Carry Select Header (Continue)

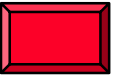


❑ Consider building a 8-bit ALU

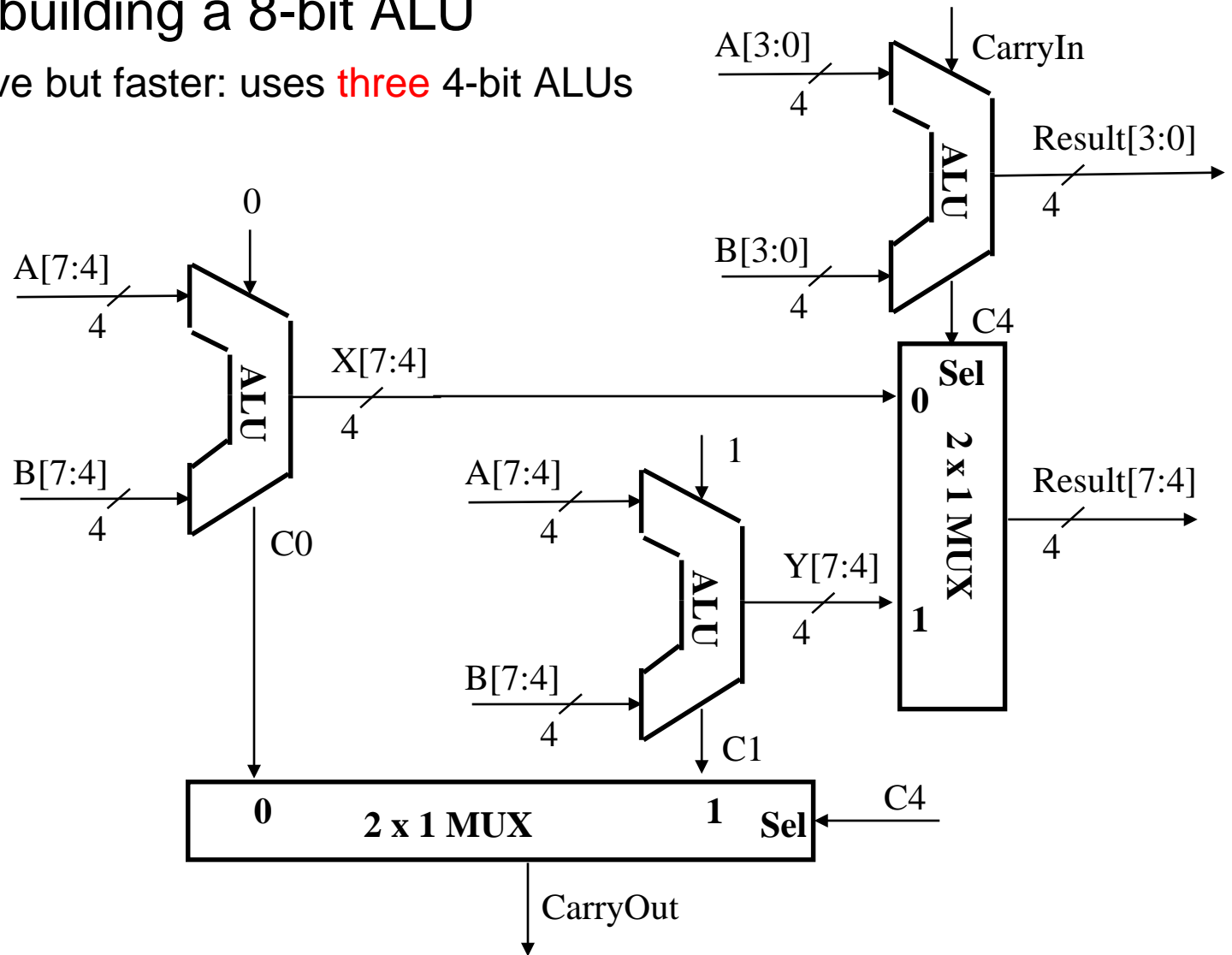- Expensive but faster: uses **three** 4-bit ALUs



The Theory Behind Carry Lookahead

 

□ Recall: $\text{CarryOut} = (B \cdot \text{CarryIn}) + (A \cdot \text{CarryIn}) + (A \cdot B)$

- $\text{Cin2} = \text{Cout1} = (B1 \cdot \text{Cin1}) + (A1 \cdot \text{Cin1}) + (A1 \cdot B1)$

- $\text{Cin1} = \text{Cout0} = (B0 \cdot \text{Cin0}) + (A0 \cdot \text{Cin0}) + (A0 \cdot B0)$

□ Substituting Cin1 into Cin2 :

- $\text{Cin2} = (A1 \cdot A0 \cdot B0) + (A1 \cdot A0 \cdot \text{Cin0}) + (A1 \cdot B0 \cdot \text{Cin0}) + (B1 \cdot A0 \cdot B0) + (B1 \cdot B0 \cdot \text{Cin0}) + (B1 \cdot A0 \cdot \text{Cin0}) + (A1 \cdot B1)$

□ Now define two new terms:

- Generate Carry at Bit i $g_i = A_i \cdot B_i$


- Propagate Carry via Bit i $p_i = A_i + B_i$

The Theory Behind Carry Lookahead (Continue)



- ❑ Using the two new terms we just defined:
 - Generate Carry at Bit i $g_i = A_i \cdot B_i$
 - Propagate Carry via Bit i $p_i = A_i + B_i$
- ❑ We can rewrite:
 - $C_{in1} = g_0 + (p_0 \cdot C_{in0})$
 - $C_{in2} = g_1 + (p_1 \cdot g_0) + (p_1 \cdot p_0 \cdot C_{in0})$
 - $C_{in3} = g_2 + (p_2 \cdot g_1) + (p_2 \cdot p_1 \cdot g_0) + (p_2 \cdot p_1 \cdot p_0 \cdot C_{in0})$
- ❑ Carry going into bit 3 is 1 if
 - We generate a carry at bit 2 (g_2)
 - Or we generate a carry at bit 1 (g_1) and bit 2 allows it to propagate (p_2 & g_1)
 - Or we generate a carry at bit 0 (g_0) and bit 1 as well as bit 2 allows it to propagate (p_2 & p_1 & g_0)
 - Or we have a carry input at bit 0 (C_{in0}) and bit 0, 1, and 2 all allow it to propagate (p_2 & p_1 & p_0 & C_{in0})

 
The Theory Behind Carry Lookahead (Continue)





A Partial Carry Lookahead Adder

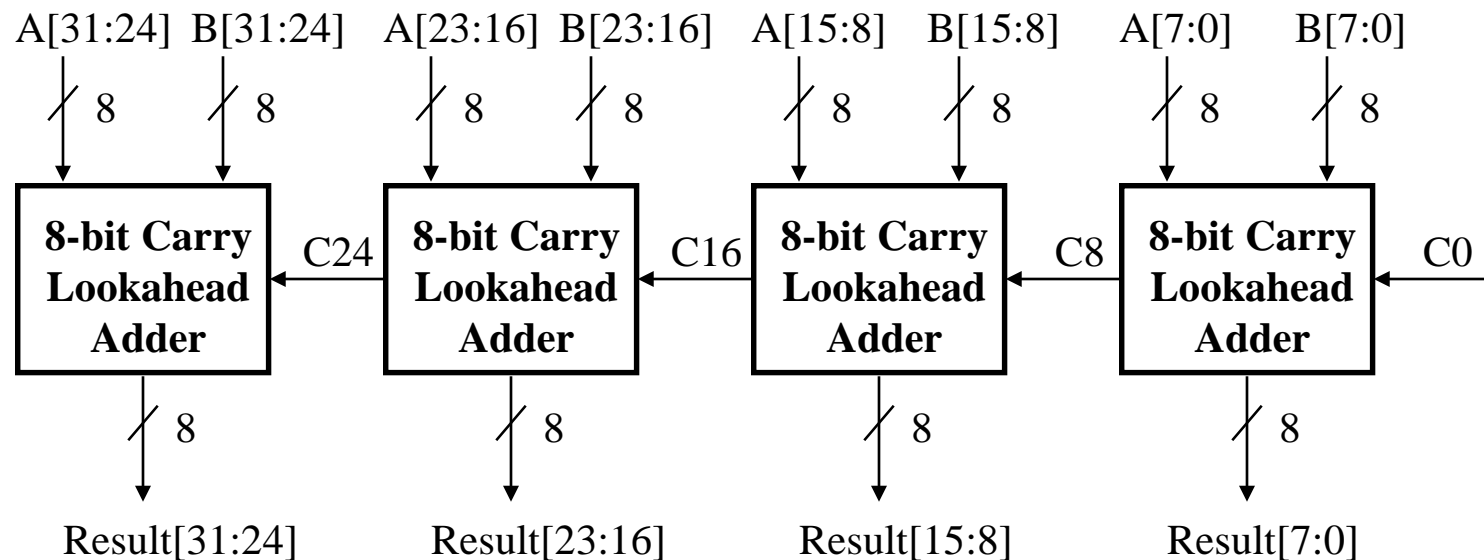- ❑ It is very expensive to build a “full” carry lookahead adder
 - Just imagine the length of the equation for C_{in31}
- ❑ Common practices:
 - Connects several N-bit Lookahead Adders to form a big adder
 - Example: connects four 8-bit carry lookahead adders to form a 32-bit partial carry lookahead adder





❑ An Overview of the Design Process

- Design is an iterative process-- successive refinement
- Do NOT wait until you know everything before you start

❑ Binary Arithmetics

- If you use 2's complement representation, subtract is easy.

❑ ALU Design

- Designing a Simple 4-bit ALU
 - How to implement SLT operation?
- Other ALU Construction Techniques