
C335

Computer Structures

Designing A MIPS Single Cycle Datapath (I)

Dr. Liqiang Zhang


Department of Computer and Information Sciences

Adapted from Morgan Kaufmann and others


The Processor: Datapath & Control




- ❑ We're ready to look at an implementation of the MIPS
- ❑ Simplified to contain only:
 - memory-reference instructions: **lw, sw**
 - arithmetic-logical instructions: **add, sub, and, or, xor, nor, slt**
 - arithmetic-logical immediate instructions: **addi, andi, ori, xori, slti**
 - control flow instructions: **beq, bne, j, (jr, jal)**
- ❑ Generic implementation:
 - use the program counter (PC) to supply the instruction address and fetch the instruction from memory (and update the PC)
 - decode the instruction (and read registers)
 - execute the instruction
 - actually include stage 3, 4, and 5 discussed in our previous lecture

 


Generic Steps of Datapath

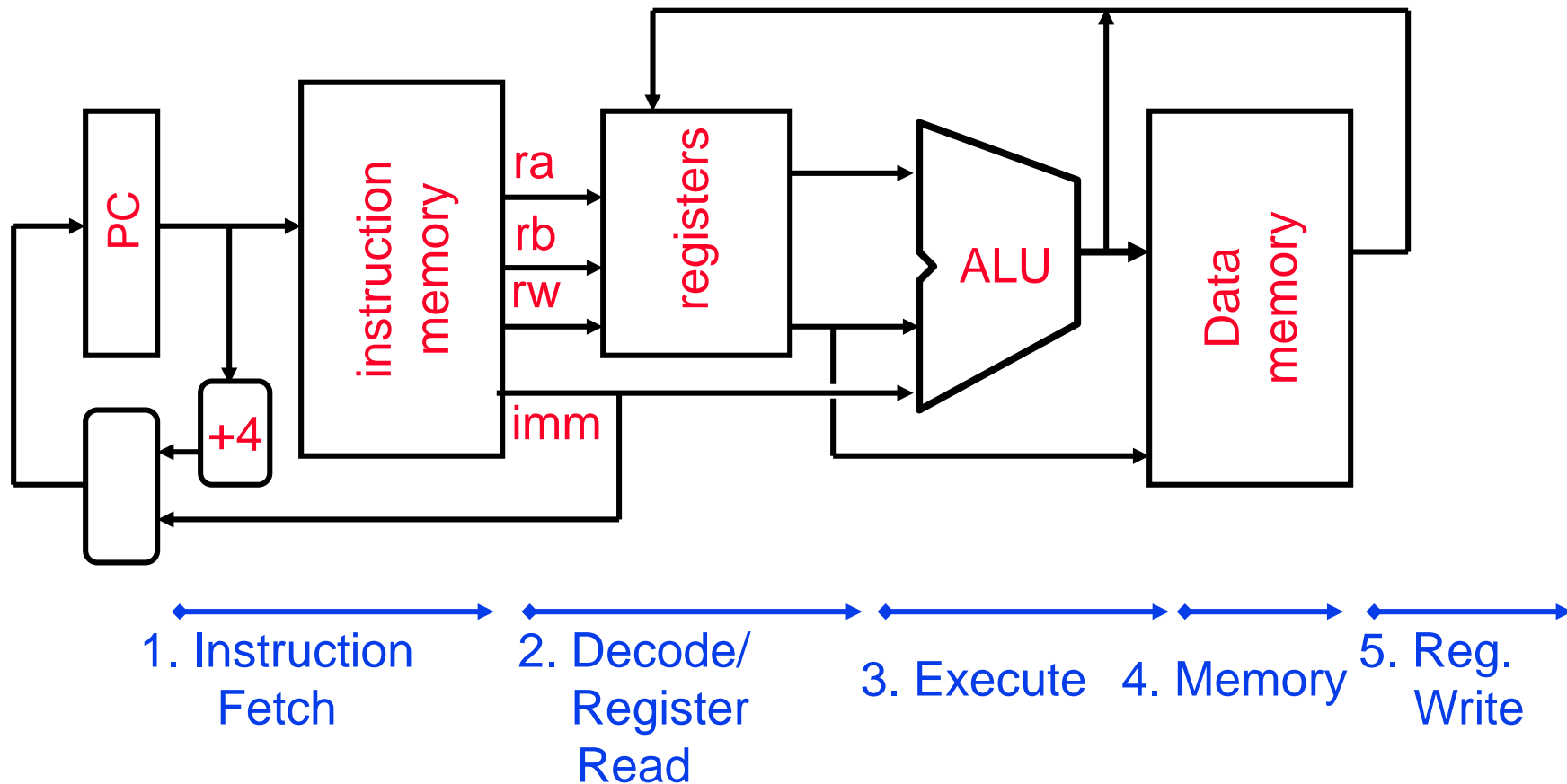

Abstract Implementation View

 

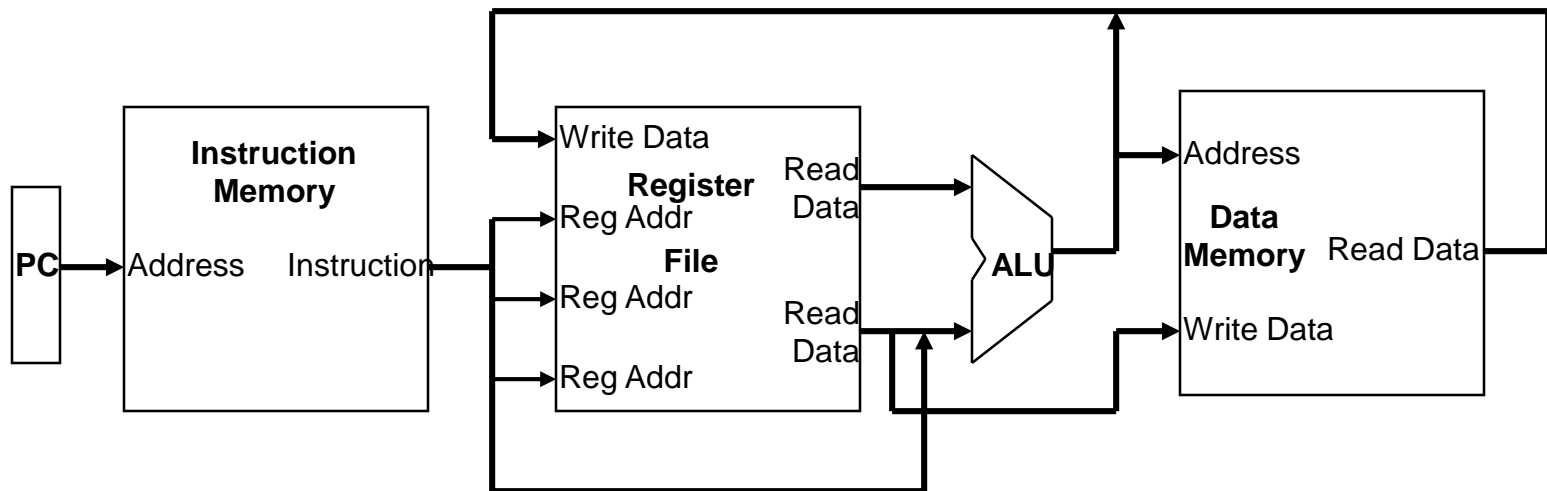
- ❑ Two types of functional units:
 - elements that operate on data values (combinational)
 - elements that contain state (sequential)




- ❑ Single cycle operation
- ❑ Split memory (**Harvard**) model - one memory for instructions and one for data

Combinational Logic Elements (Building Blocks)


□ Adder

 

□ MUX

 

□ ALU

 

Combinational Logic vs. Sequential Logic



□ Combinational logic:

- the output of the logic device is dependent only on the present inputs to the device.
- Examples: adder, multiplex, decoder, ALU (without considering the registers)


□ Sequential logic

- the output of the logic device is dependent **not only** on the present inputs to the device, **but also** on past inputs;
- i.e., the output of a sequential logic device depends on its present internal state and present inputs.
- It has some kind of **memory** of at least part of its “history”
- It contains **state element(s)**
- Examples: latches, flip flops, registers, memory, counters...


Latches and Flip Flops – The Simplest State Elements




□ The D Latch and the D Flip Flop

 

\overline{Preset}	\overline{Clear}	Clock	D	Q	\overline{Q}
0	1	x	x	1	0
1	0	x	x	0	1
0	0	x	x	1	1
1	1	\uparrow or 1	0	0	1
1	1	\uparrow or 1	1	1	0
1	1	0	X	Q_0	\overline{Q}_0

 

(a) The D latch

 


(b) The D flip flop

The Timing Diagram of D Latch and D Flip Flop

Exercise

❑ Complete the timing diagram


 


Latches vs Flipflops



- ❑ Output is equal to the stored value inside the element
- ❑ Change of state (value) is based on the clock
 - **Latches**: output changes whenever the inputs change and the clock is asserted (level sensitive methodology)
 - **Flip-flops**: output changes only on a clock edge (edge-triggered methodology)
- ❑ There are other type of flip flops: **RS, JK, T**.
However, D type is the only type that we need in this class.

Clocking Methodologies

 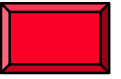


clock rate = $1/(\text{clock cycle})$

e.g., 10 nsec clock cycle = 100 MHz clock rate


1 nsec clock cycle = 1 GHz clock rate


- ❑ Clocking methodology defines when signals (data) can be read and when they can be written
 - For edge-triggered clocking, when used for data writing, the clock edge acts a sampling signal causing the value of the data input to a state element to be sampled and stored in the state element.
- ❑ State element design choices
 - level sensitive latch
 - edge-triggered flipflops

State Element: Register (Building Block)

 

 - Similar to D Flip Flop except
 - N-bit input and output
 - Write Enable input
- RegWrite:
 - negated (or deasserted) (0):
Data Out will not change
 - asserted (1):
Data Out will become Data In on positive edge of clock



 

State Element: Register File

❑ Register File consists of 32 registers:


- Two 32-bit output busses: busA and busB
- One 32-bit input bus: busW

❑ Register is selected by:



- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when RegWrite is 1

❑ Clock input (clk)



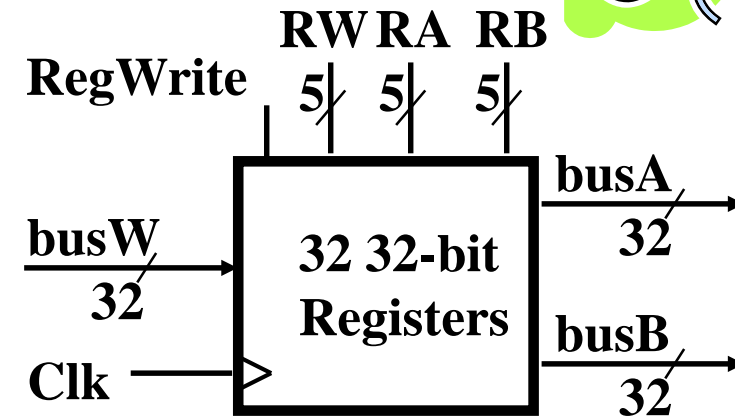
- The clk input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after “access time.”



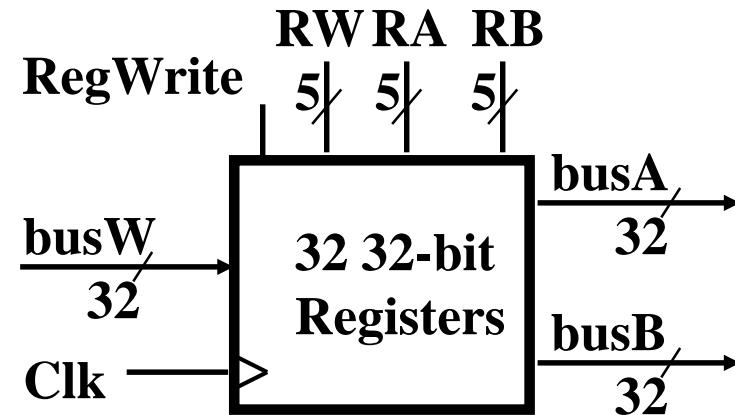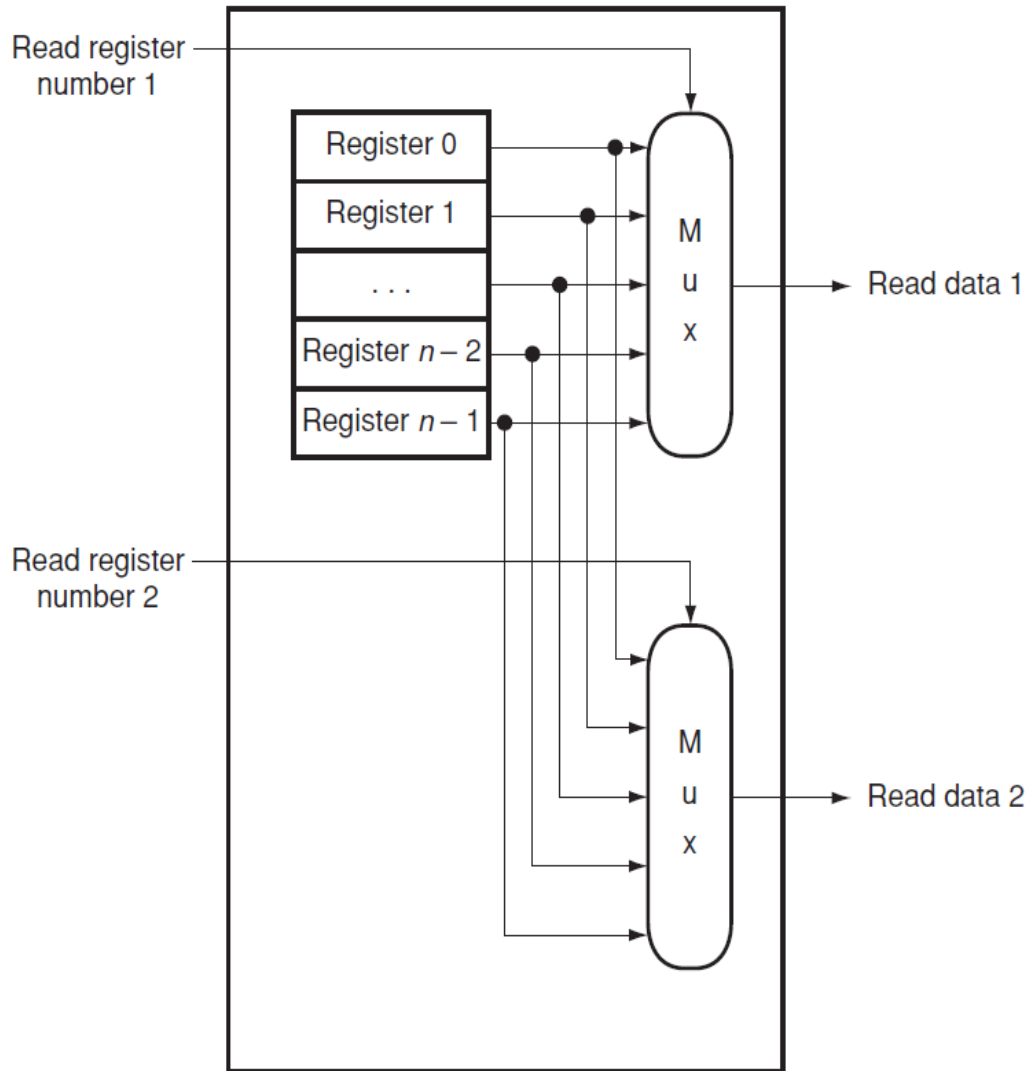
Register File – Read Ports Implementation



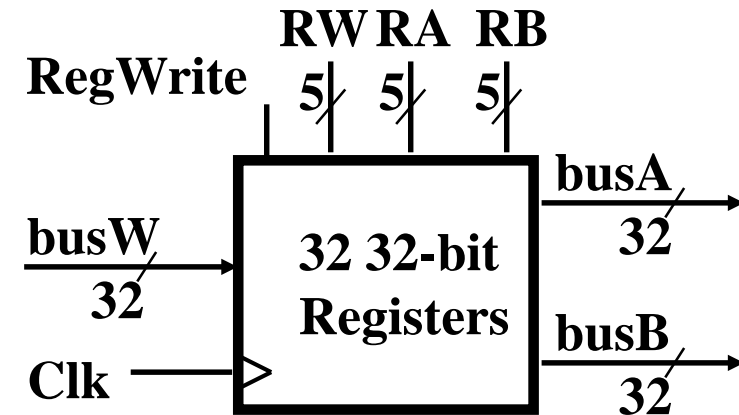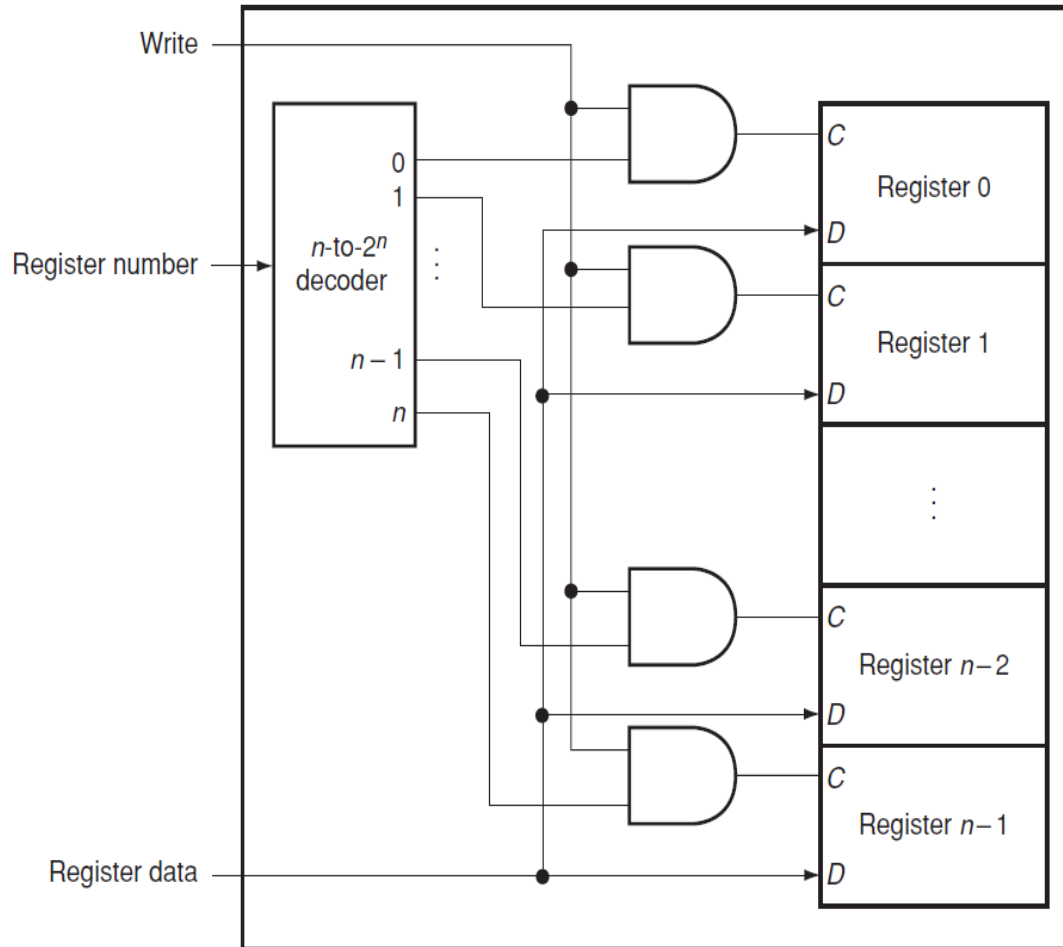 Register File – Write Port Implementation




State Element: Idealized Memory

 

❑ Memory (idealized)

 - One input bus: Data In
- One output bus: Data Out



❑ Memory word is selected by:

- MemRead = 1: address selects the word to put on Data Out
- MemWrite = 1: address selects the memory word to be written via the Data In bus


❑ Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - Address valid & MemRead (asserted) \Rightarrow Data Out valid after “access time.”



Our Implementation

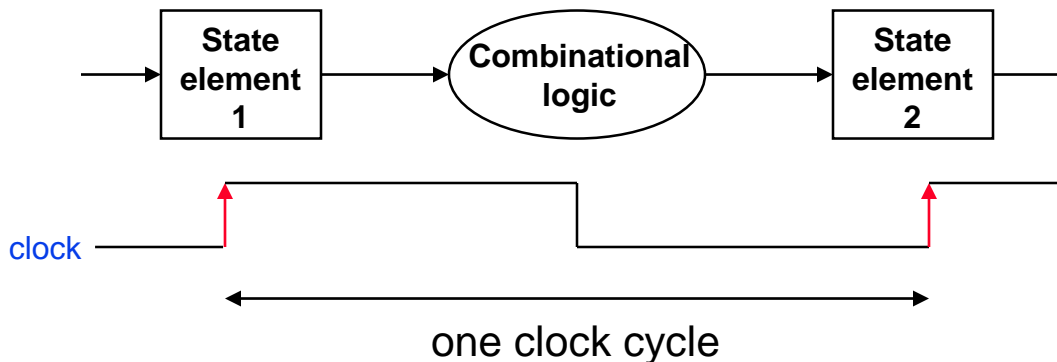- ❑ An edge-triggered methodology
- ❑ Typical execution
 - read contents of some state elements
 - send values through some combinational logic
 - write results to one or more state elements





- ❑ Assumes state elements are written on every clock cycle; if not, need explicit write control signal
 - write occurs only when **both** the write control is asserted and the clock edge occurs

Fetching Instructions



❑ Fetching instructions involves

  - reading the instruction from the Instruction Memory
- updating the PC value to be the address of the next (sequential) instruction




- PC is updated every clock cycle, so it does not need an explicit write control signal
- Instruction Memory is read every clock cycle, so it doesn't need an explicit read control signal

Decoding Instructions




❑ Decoding instructions involves

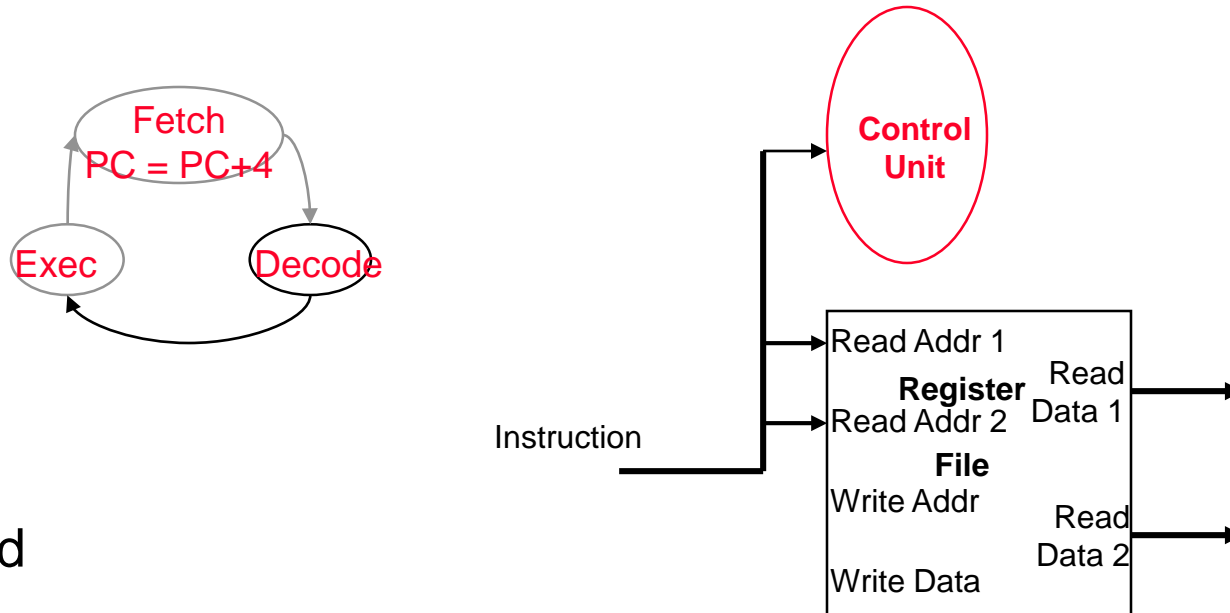- sending the fetched instruction's opcode and function field bits to the control unit



- reading two values from the Register File
 - Register File addresses are contained in the instruction

Reading Registers “Just in Case”

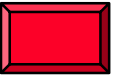

- ❑ Note that both RegFile read ports are active for **all** instructions during the Decode cycle using the rs and rt instruction field addresses
 - Since haven't decoded the instruction yet, don't know what the instruction is !
 - *Just in case* the instruction uses values from the RegFile do “work ahead” by reading the two source operands

Which instructions *do* make use of the RegFile values?


- ❑ Also, all instructions (except **Jump** instructions) use the ALU **after** reading the registers

Why? memory-reference? arithmetic? control flow?



Executing R Format Operations



 □ R format operations (**add, sub, slt, and, or**)



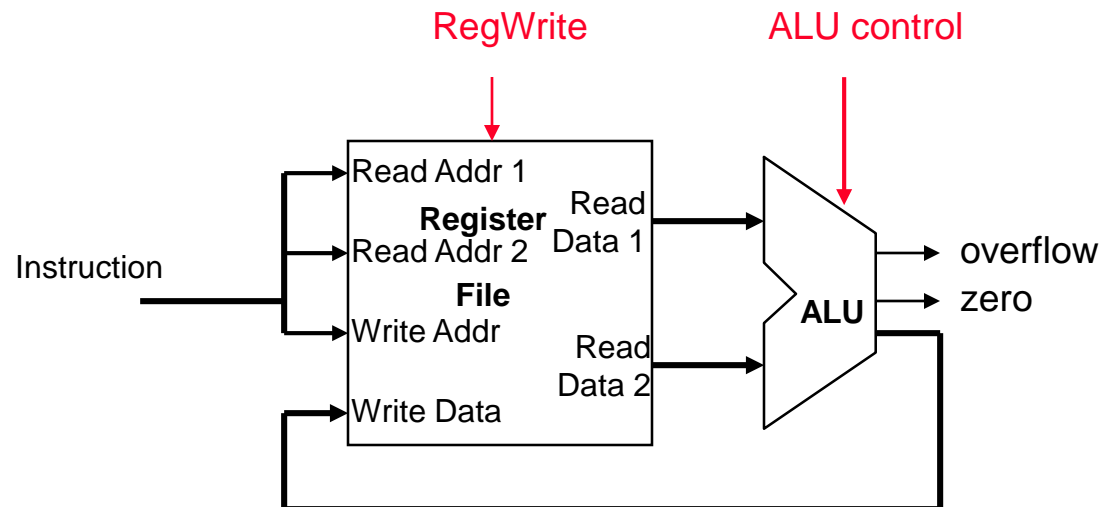 - perform operation (**op** and **funct**) on values in **rs** and **rt**
- store the result back into the Register File (into location **rd**)




- Note that Register File is not written every cycle (e.g. **sw**), so we need an explicit write control signal for the Register File

Consider the `slt` Instruction

- Remember the R format instruction `slt`

```
slt $t0, $s0, $s1  # if $s0 < $s1
                   #      then $t0 = 1
                   #      else $t0 = 0
```

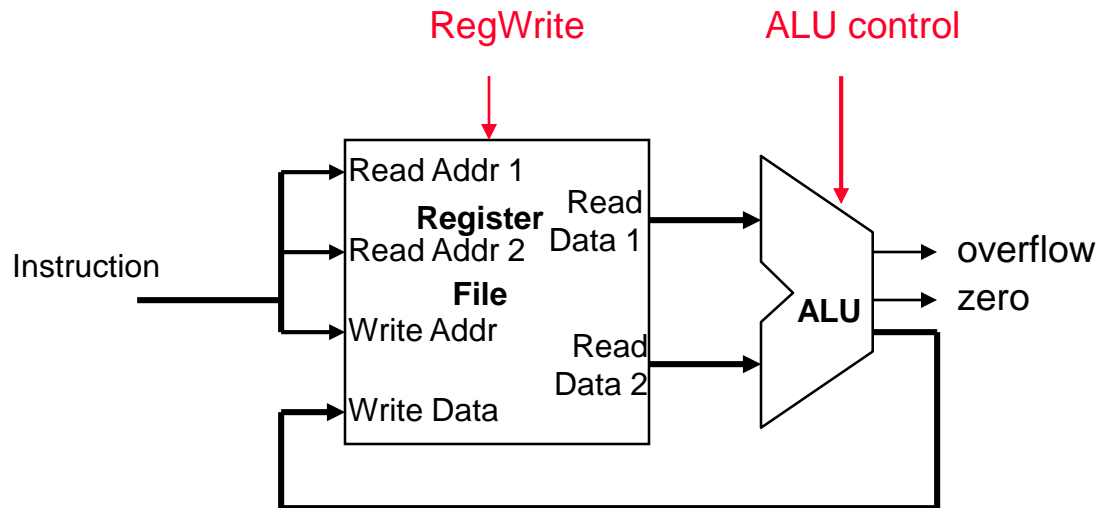
- Where does the 1 (or 0) come from to store into `$t0` in the Register File at the end of the execute cycle?



Executing Load and Store Operations




□ Load and store operations have to

 

- compute a memory address by adding the base register (in **rs**) to the 16-bit signed offset field in the instruction
 - base register was read from the Register File during decode
 - offset value in the low order 16 bits of the instruction must be sign extended to create a 32-bit signed value
- **store** value, read from the Register File during decode, must be written to the Data Memory
- **load** value, read from the Data Memory, must be stored in the Register File

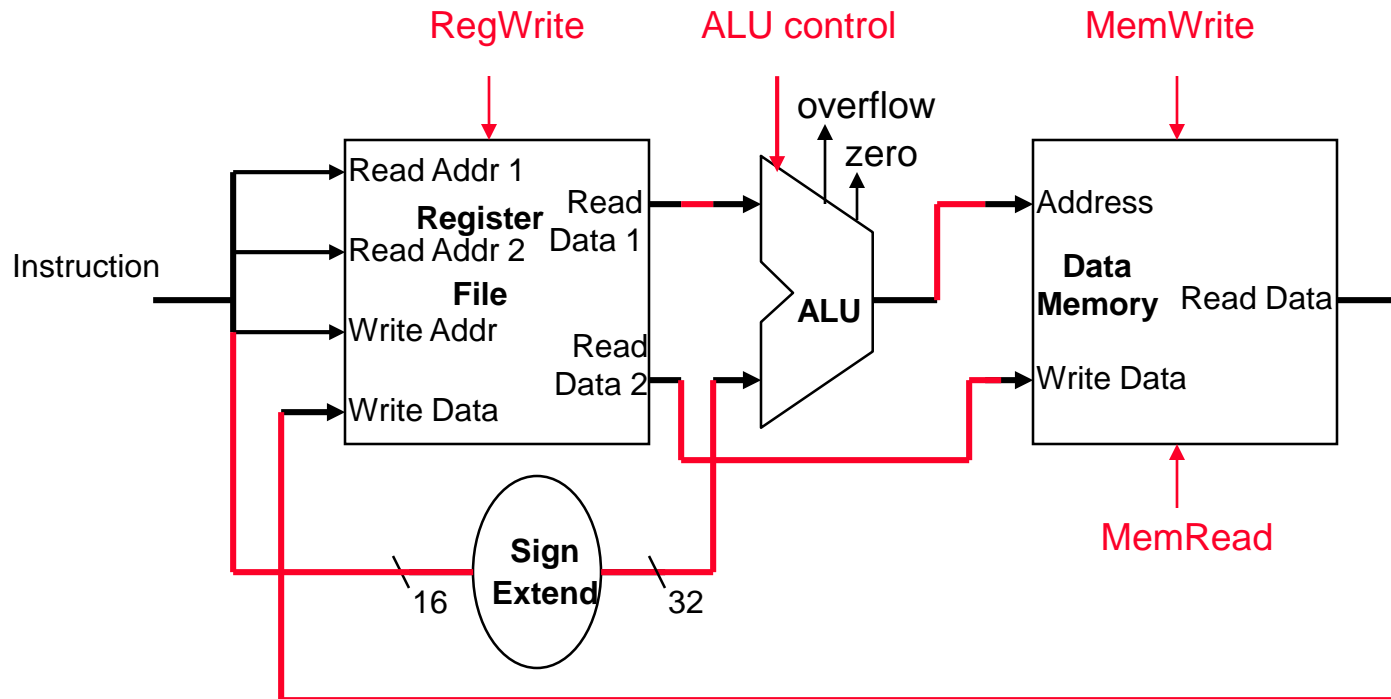
Executing Load and Store Operations, (con't)



Executing Branch Operations




- ❑ Branch operations have to

 


- compare the operands read from the Register File during decode (**rs** and **rt** values) for equality (**zero** ALU output)
- compute the branch target address by adding the updated PC to the sign extended 16-bit signed offset field in the instruction
 - “base register” is the **updated** PC
 - offset value in the low order 16 bits of the instruction must be sign extended to create a 32-bit signed value and then shifted left 2 bits to turn it into a word address

Executing Branch Operations (con't)

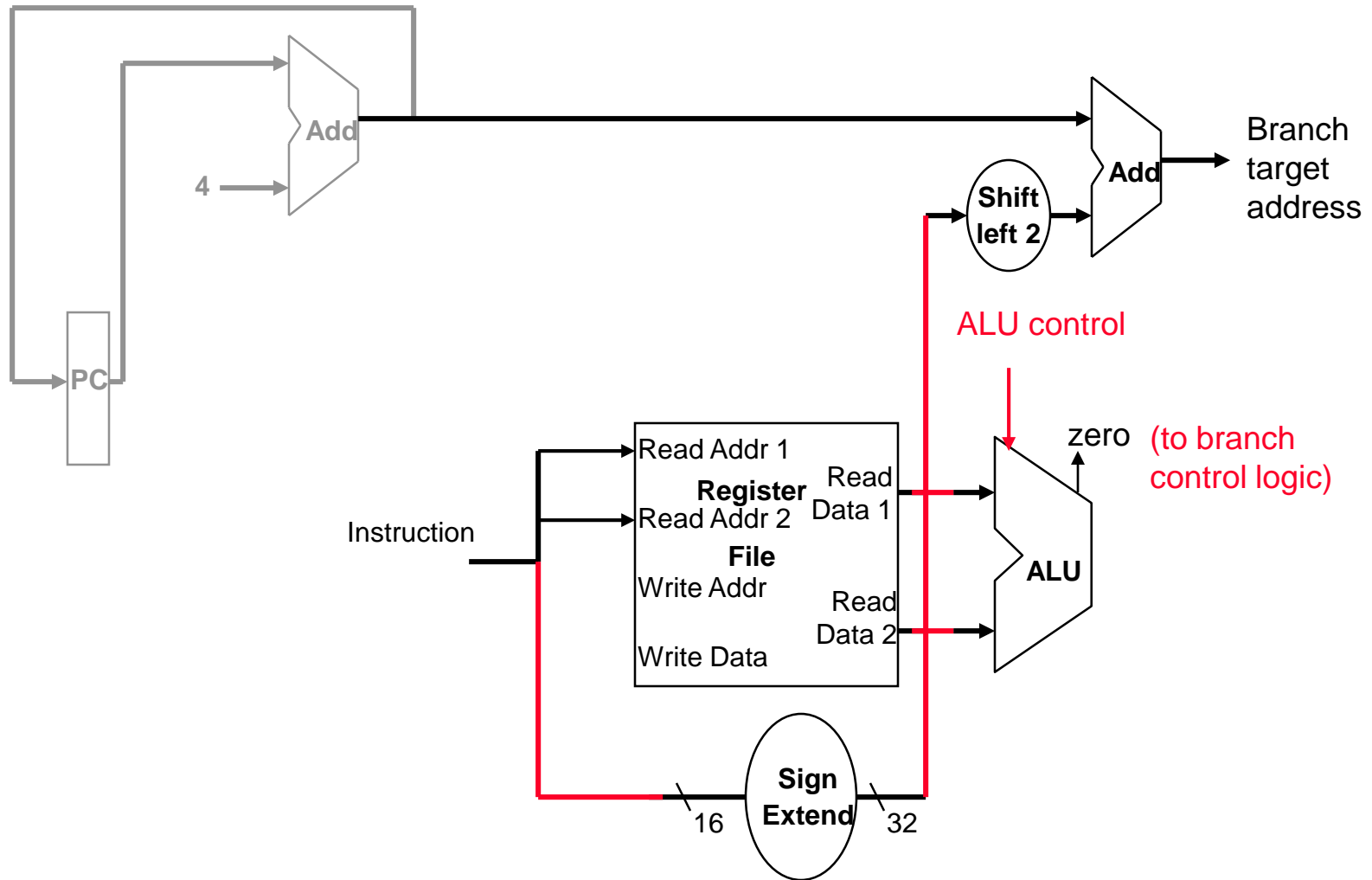


Executing Jump Operations

 


- Jump operations have to



 - replace the lower 28 bits of the PC with the lower 26 bits of the fetched instruction shifted left by 2 bits




 Creating a Single Datapath from the Parts




- ❑ Assemble the datapath elements, add control lines as needed, and design the control path
- ❑ Fetch, decode and execute each instructions in one clock cycle – **single cycle** design
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., why we have a separate Instruction Memory and Data Memory)
 - to share datapath elements between two different instruction classes will need **multiplexors** at the input of the shared elements with control lines to do the selection
- ❑ Cycle time is determined by length of the longest path


Fetch, R, and Memory Access Portions

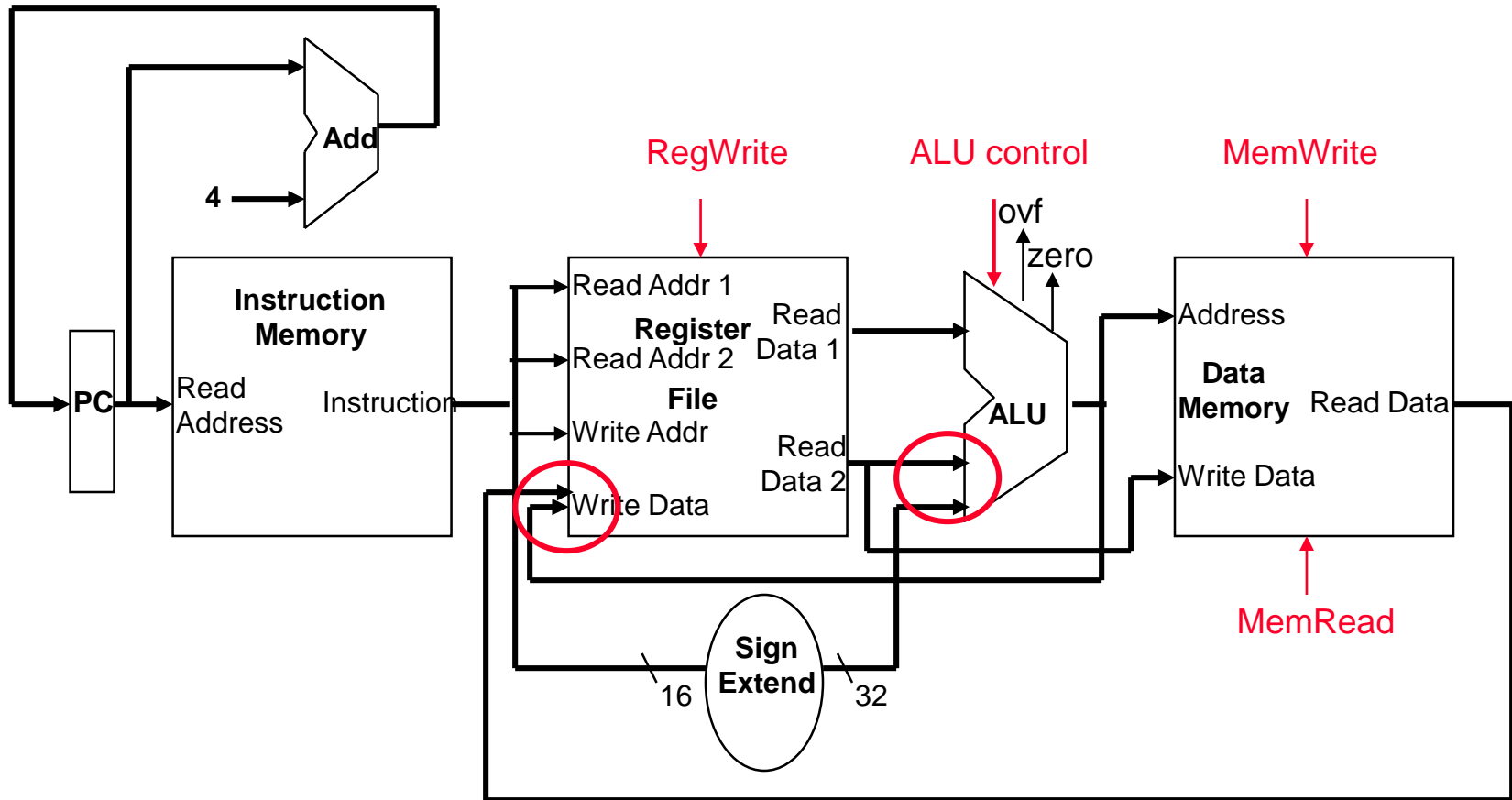


Multiplexor Insertion

 

Adding the Branch Portion

 

Our Simple Control Structure


 


- ❑ We wait for everything to settle down
 - ALU might not produce “right answer” right away
 - Memory and RegFile reads are combinational (as are ALU, adders, muxes, shifter, signextender)
 - Use write signals along with the clock edge to determine when to write to the sequential elements (to the PC, to the Register File and to the Data Memory)

- ❑ The clock cycle time is determined by the logic delay through the longest path

We are ignoring some details like register
setup and hold times

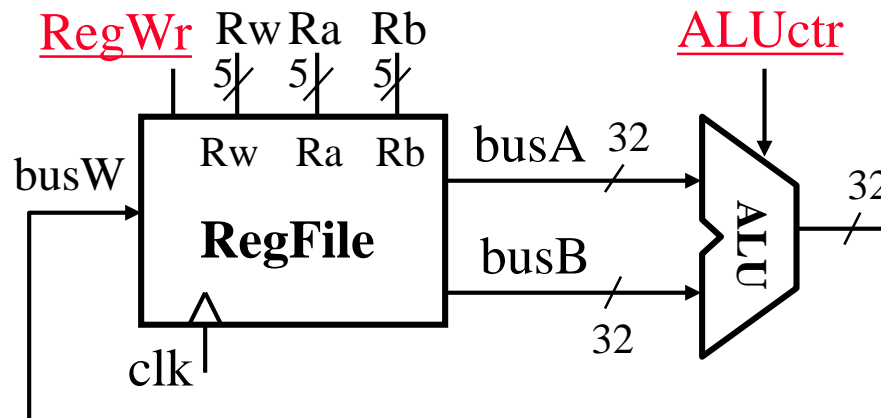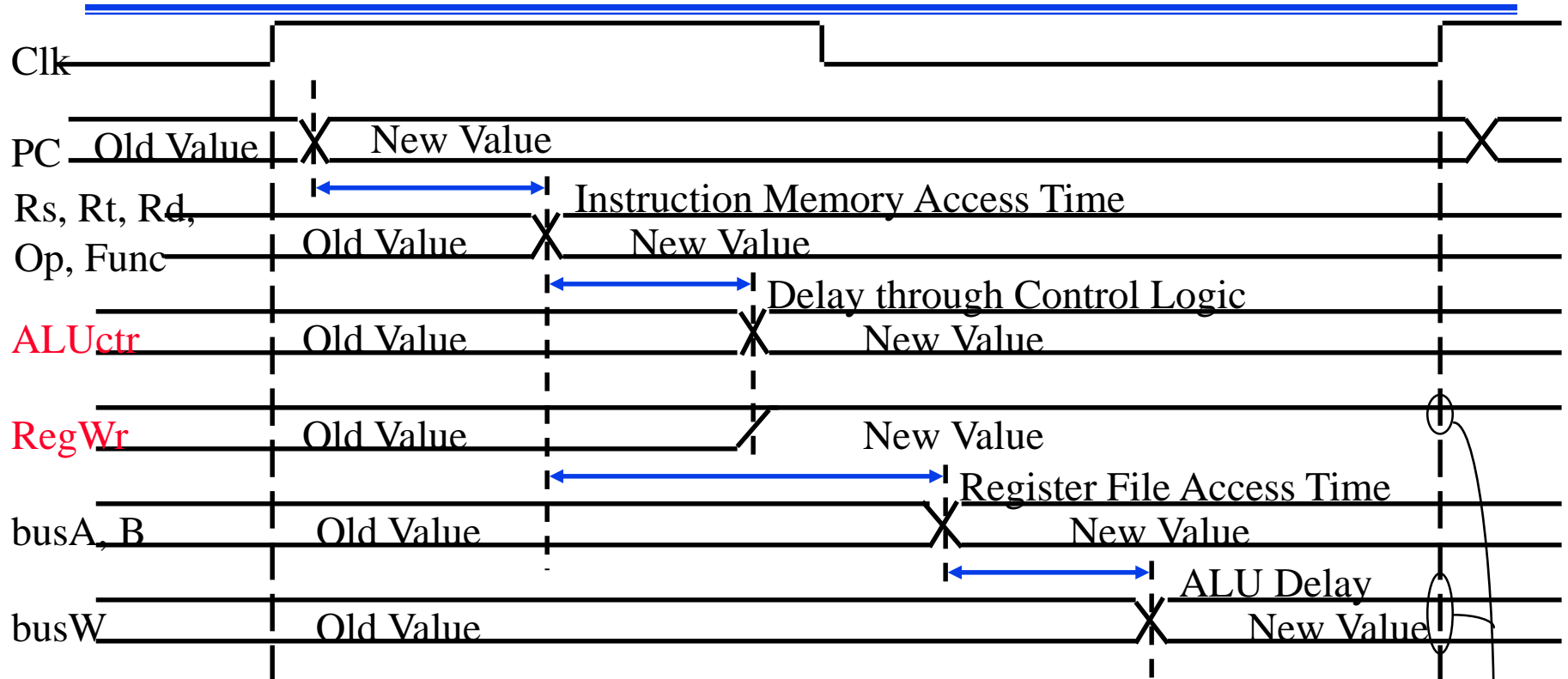Register-Register Timing: One complete cycle



**Register Write
Occurs Here**